

ELECTRONICS AND COMMUNICATION ENGINEERING

QUESTION BANK

Course Title: Electronics Devices and Circuits

Course Code: 25EC303

Regulation : NR25

Course Outcomes (CO's)

CO1: Analyze the electronic characteristics and models of semiconductor diode and apply them in rectifier and clipping circuits

CO2: Evaluate the operation and configurations of Bipolar Junction Transistors (BJTs) and Analyze their input and output characteristics

CO3: Design appropriate biasing networks for BJTs and determine the operating point for Amplifier applications

CO4: Analyze transistor amplifier circuits using h-parameter models and assess Performance for various configurations.

CO5: Analyze the structure, working, and characteristics of JFETs, MOSFETs, and Advanced Devices like Fin FETs and CNTFETs, and compare modern device Technologies

UNIT-I

DIODE CHARACTERISTIC AND APPLICATIONS

S.No	Questions	BT	CO	PO
Part –A(Short Answer Questions)				
1	Define Static and Dynamic resistance of PN Diode?	L2	1	2
2	What is meant by depletion region?	L2	1	1
3	Determine the forward resistance of PN junction diode. When the forward current is 5mA at T=300K assume is diode.	L2	1	1
4	Write the effect of temperature on diode characteristics?	L4	1	2
5	A silicon diode has a saturation current of 7.5μ A at room temperature 300K.calculate the saturation current at 400K.	L3	1	2
6	Draw the Diode Equivalent Circuit. Mention the applications of PN-junction diode.	L3	1	1
7	Define ripple factor and PIV	L4	1	1
8	Define diffusion capacitance and its formulae.	L2	1	1
9	Define transition capacitance and its formulae.	L2	1	1
10	Define PN junction diode and draw its symbol.	L2	1	1
11	Define drift and diffusion currents?	L2	1	1
12	What is meant by avalanche breakdown in PN junction diode?	L2	1	1
13	What is a rectifier and its types?	L2	1	1
14	What do you mean by positive and negative clamping?	L2	1	1

Part– B(Long Answer Questions)					
15	a)	The reverse saturation current of a silicon p-n junction diode at an operating temperature of 27°C is 50 nA. Compute the dynamic forward and reverse resistances of the diode for applied voltages of 0.8 V and -0.4 V respectively.	L3	1	1, 2
	b)	Obtain the transition capacitance (C_T) of a junction diode at a reverse bias voltage of 12 V if (C_T) is 15 pF at a reverse bias of 8 V. Differentiate between transition and diffusion capacitances.	L3, L4	1	1, 2
16	a)	Define the following terms of a rectifier: (i) Ripple Factor (ii) Regulation (iii) Rectification Efficiency (iv) Form Factor	L1	1	1
	b)	What is the ripple factor if a power supply of 220 V, 50 Hz is to be Full Wave rectified and filtered with a 220 μ F capacitor before delivering to a resistive load of 120 Ω ? Compute the value of the capacitor for the ripple factor to be less than 15%.	L3	1	1, 2
17	a)	Derive expressions for ripple factor of a Full Wave Rectifier with and without a capacitive filter.	L4	1	1, 2
	b)	Define the following terms and derive the equations with respect to half-wave rectifier: (i) Ripple factor (ii) Peak inverse voltage (iii) Rectification efficiency (iv) % Regulation	L4	1	1, 2
18	a)	The reverse saturation current of a silicon p-n junction diode at an operating temperature of 27°C is 50 nA. Compute the dynamic forward and reverse resistances of the diode for applied voltages of 0.8 V and -0.4 V respectively.	L3	1	1, 2
	b)	Explain the V-I characteristics of a PN junction diode.	L3	1	3
19	a)	Derive the expression for dynamic resistance of a diode.	L3	1	2
	b)	Explain transition capacitance and diffusion capacitance with suitable expressions.	L4	1	2
20	a)	Explain Ideal, Simplified and Piecewise Linear diode models.	L3	1	1
	b)	Explain the operation of a Half-Wave Rectifier with circuit diagram and waveforms.	L3	1	3
21	a)	Derive the ripple factor, rectification efficiency and PIV of a Half-Wave Rectifier.	L4	1	3
	b)	Explain the operation of a Centre-Tapped Full-Wave Rectifier with circuit diagram and waveforms.	L3	1	3
22	a)	Explain the operation of a Bridge Rectifier with circuit diagram and waveforms.	L3	1	3

	b)	Compare Half-Wave, Centre-Tapped Full-Wave and Bridge Rectifiers.	L4	1	2
23	a)	Derive the ripple factor and rectification efficiency of a Full-Wave Rectifier.	L4	1	3
	b)	Explain the working of a capacitor filter with circuit diagram and waveforms.	L3	1	3
24	a)	Explain diode conducting and non-conducting intervals in a capacitor filter.	L4	1	2
	b)	Derive the ripple factor of a Full-Wave Rectifier with capacitor filter.	L4	1	3
25	a)	Explain the operation of positive and negative clipper circuits with waveforms.	L3	1	3
	b)	Explain the operation of positive and negative clamper circuits with waveforms.	L3	1	3
26	a)	Explain the V-I characteristics of a Zener diode.	L3	1	2
	b)	Explain Zener and Avalanche breakdown mechanisms in detail.	L4	1	2
27	a)	Explain the operation of a Zener diode as a voltage regulator.	L3	1	3
	b)	Compare PN junction diode and Zener diode.	L4	1	2
28		Explain the V-I characteristics of a PN junction diode.	L3	1	3