

 NARSIMHA REDDY ENGINEERING COLLEGE UGC AUTONOMOUS INSTITUTION Your roots to success...	NARSIMHA REDDY ENGINEERING COLLEGE UGC AUTONOMOUS INSTITUTION		UGC - Autonomous Institute Accredited by NBA & NAAC with 'A' Grade Approved by AICTE Permanently affiliated to JNTUH
	Maisammaguda (V), Kompally - 500100, Secunderabad, Telangana State, India		
	QUESTIONBANK		
	UNIT-II		

QUESTIONBANK

UNIT-II

S.No	Questions	BT	CO	PO
Part- A(Short Answer Questions)				
1	What is a BJT and draw its symbol.	2	2	1
2	What do you mean by early effect.	1	2	1
3	Compare CE, CB and CC configurations	2	2	1
4	Which of the BJT configurations are suitable for impedance matching applications? Why?	2	2	1
5	Write a short notes on switching characteristics of a transistor	2	2	1
6	Write a short note on transistor as a switch	4	2	2
7	What are the three regions of a transistor?	2	2	2
8	In a CB transistor circuit the emitter current I_E is 10mA and collector current is 9.8mA. find the value of the base current I_B	2	2	1
9	If a transistor has α of 0.97, find the value of β . If $\beta=200$, find the value of α .	2	2	1
10.	Define ON time and OFF time of a transistor.	2	2	1
11.	How are the junctions of a transistor biased for saturation region operation?	1	2	1
12.	When does a transistor act as (a) a closed switch and (b) an open switch?	1	2	1
13.	When the emitter current of a transistor is changed by 1mA, there is a change in collector current by 0.99 mA. Find the current gain of the transistor.	2	2	1
14.	Why we call BJT is a current controlled device?	2	2	1
Part- B(Long Answer Questions)				
15	(a) With neat diagram explain various current components in an PNP/NPN bipolar junction transistor.	3	2	1
	(b) Explain the working of a transistor as a switch.			
16	(a) Draw and explain input and output characteristics of CB configuration	2	2	1
17	a) Draw and explain input and output characteristics of CE configuration	4	2	2
	b) Explain the different operating regions of transistor.	2	2	3
18	a) Draw and explain working principle of CC characteristics of a transistor.	3	2	3
	b) Give the relationship between alpha, beta and gamma of BJT.	2	2	2