



NARSIMHA REDDY ENGINEERING COLLEGE

UGC AUTONOMOUS INSTITUTION

Maisammaguda (V), Kompally - 500100, Secunderabad, Telangana State, India

UGC - Autonomous Institute
Accredited by NBA & NAAC with 'A' Grade
Approved by AICTE
Permanently affiliated to JNTUH

UNIT-III

| S.No | Questions | BT | CO | PO |
|---------------------------------------|---|----|----|-------|
| Part-A(Short Answer Questions) | | | | |
| 1 | What is bias? what is the need for biasing | 2 | 3 | 1 |
| 2 | What are the conditions for operating point? | 3 | 3 | 1,2 |
| 3 | Draw a small signal low frequency model of a transistor? | 2 | 3 | 1,2 |
| 4 | Mention important characteristics of CE amplifier? | 2 | 3 | 1,2,3 |
| 5 | Write the typical values of transistor configuration in h-parameter model. | 3 | 3 | 1,2 |
| 6 | Explain thermal stability? | 2 | 3 | 1,2 |
| 7 | Compare the three biasing circuits | 3 | 3 | 1,2 |
| 8 | What is the need for biasing ? | 2 | 3 | 1,2 |
| 9 | Explain, How to avoid the thermal runaway? | 2 | 3 | 1,2 |
| 10 | Define the stability factor for Fixed bias circuit, collector to base bias, voltage divider bias circuit? | 2 | 3 | 1,2 |
| Part-B(Long Answer Questions) | | | | |
| 11 | a) Draw the fixed bias circuit and derive the stability factor. | 2 | 3 | 1 |
| 12 | a) Discuss the low frequency response of BJT amplifier and the effect of coupling and bypass capacitors. | 2 | 3 | 1,2 |
| | b) What is transistor amplifying action? | 3 | 3 | 1,2 |
| 13 | Explain AC and DC load line analysis in BJT and discuss the criteria for fixing the Q-point. | 2 | 3 | 1,2,3 |
| 14 | Explain the h-parameter equivalent circuit for a typical common emitter amplifier and derive expression for A_i and A_v . | 2 | 3 | 1,2 |
| 15 | What is the necessity of biasing circuits? Derive the expression for stability factor of a self bias circuit? | 2 | 3 | 1,2 |
| 16 | In a silicon transistor circuit with a fixed bias, $V_{CC}=9V$, $R_C=3K\Omega$, $R_B=8K\Omega$, $\beta=50$, $V_{BE}=0.7V$ find the operating point and stability factor | 2 | 3 | 1,2 |
| 17 | Explain the need for biasing circuit? Describe about the factors affecting the operating point | 2 | 3 | 1,2 |
| 18 | Derive the stability factor for a fixed bias circuit | 3 | 3 | 1,2 |
| 19 | Derive the stability factor for a voltage divider bias circuit | 3 | 3 | 1,2 |
| 20 | Design the voltage divider circuit from the following Data $V_{CC} = 24V$, $\beta = 110$, $I_{CQ} = 4mA$, $V_{CEQ} = 8V$ and choose $V_E = V_{CC}/8$. | 3 | 3 | 1,2 |