



### UNIT-IV

| S.No                          | Questions   |   | BT | CO | PO    |
|-------------------------------|---|---|----|----|-------|
| Part–A(ShortAnswer Questions) |   |   |    |    |       |
| 1                             | Define small-signal analysis and explain its purpose.   |   | 2  | 4  | 1     |
| 2                             | State the conditions required for a transistor to operate under small-signal mode.                            |   | 3  | 4  | 1,2   |
| 3                             | What is trans conductance ( $g_m$ , $g_{m\pi}$ )? Give its formula.   |   | 2  | 4  | 1,2   |
| 4                             | Mention important characteristics of CE amplifier?  |   | 2  | 4  | 1,2,3 |
| 5                             | Draw the small-signal hybrid- $\pi$ model of a BJT..  |   | 3  | 4  | 1,2   |
| 6                             | Draw the CE amplifier circuits and its H Parameter equivalent circuit   |   | 3  | 4  | 1,2   |
| 7                             | Write the CE amplifier current gain ,voltage Gain, Input impedance, output impedance in terms of H parameters |   | 2  | 4  | 1,2   |
| 8                             | What is the Amplifier? List the classification of Amplifier?  |   | 2  | 4  | 1,2   |
| 9                             | Draw the CB Amplifier & Its Hybrid equivalent circuit   |   | 3  | 4  | 1,2   |
| 10                            | Draw the CC Amplifier & Its Hybrid equivalent circuit   |   | 3  | 4  | 1,2   |
| Part–B(LongAnswerQuestions)   |   |   |    |    |       |
| 11                            | a)  | Explain two-port network h-parameter models. Draw CE, CB, and CC h-models and discuss their utility.  | 2  | 4  | 1     |
| 12                            | a)  | Discuss the low frequency response of BJT amplifier and the effect of coupling and bypass capacitors.   | 2  | 4  | 1,2   |
|                               | b)  | What is transistor amplifying action?   | 3  | 4  | 1,2   |
| 13                            |   | Compare CE, CB, and CC amplifiers based on: Voltage gain, current gain, impedance levels, phase shift, applications.  | 2  | 4  | 1,2,3 |
| 14                            |   | Explain the h-parameter equivalent circuit for a typical common emitter amplifier and derive expression for $A_i$ and $A_v$ .   | 2  | 4  | 1,2   |
| 15                            |   | Explain the Approximation of CE model with Neat Sketch  | 2  | 4  | 1,2   |
| 16                            |   | Explain the Small signal Analysis of single stage CE Amplifier with fixed Bias and derive the input impedance, output impedance current gain  | 2  | 4  | 1,2   |
| 17                            |   | Explain the Small signal Analysis of single stage CE Amplifier with unbiased emitter resistor and derive the input impedance, output impedance current gain   | 2  | 4  | 1,2   |
| 18                            |   | Explain the Small signal Analysis of single stage CB Amplifier with unbiased emitter resistor and derive the input impedance, output impedance current gain   | 2  | 4  | 1,2   |
| 19                            |   | A CE amplifier is drawn by a voltage source of internal resistance $R_S = 800$ ohms and load impedance is a resistance $R_L = 1000$ ohms. The h-parameters are $h_{ie} = 1.0$ K ohms, $h_{re} = 2 \times 10^{-4}$ , $h_{fe} = 50$ and $h_{oe} = 25 \mu A/V$ . compute $A_i$ , $R_i$ , $A_v$ , $R_o$ using exact analysis. | 3  | 4  | 1,2   |