

Introduction to Digital Systems

Digital systems are the foundation of modern technology, enabling the processing, storage, and transmission of information in the form of discrete signals. This course will provide a comprehensive understanding of the principles and applications of digital systems, laying the groundwork for a career in computer engineering or electronics.


Digital Circuits and Systems

Section 1 - Combinatorial Logic

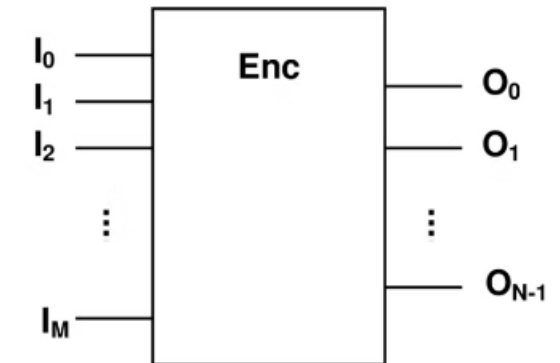1.1 Encoders:

Definition

- An encoder produces a digital code which depends on which one of its input is activated



- Only one of M inputs is activated at a time
- Encoder outputs a N-bit output code
- Always: $2^N \geq M$

Example



Binary Number System

Fundamentals

The binary number system uses only two digits, 0 and 1, to represent all numerical values. This system is the foundation of digital electronics and computer programming.

Advantages

Binary numbers are well-suited for digital systems because they can be easily represented and manipulated using electronic circuits and components.

Applications

Binary numbers are used extensively in computer memory, data storage, and digital signal processing, enabling the efficient storage and processing of information.


$$0 \times 8 = 0$$

$$1 \times 16 = 16$$

Decimal to Binary Conversion

Step 1

Divide the decimal number by 2 and record the remainder.

1

2

Step 2

Divide the result from Step 1 by 2 and record the remainder.

Step 3

Repeat Step 2 until the result is 0. The binary number is the sequence of remainders in reverse order.

3

Binary to Decimal Conversion

1 Multiply Each Digit

Multiply each binary digit by the corresponding power of 2, starting from the rightmost digit.


2 Sum the Results

Add up all the results to get the decimal equivalent.

3 Example


The binary number 1010 is equal to $(1 \times 2^3) + (0 \times 2^2) + (1 \times 2^1) + (0 \times 2^0) = 8 + 0 + 2 + 0 = 10$.

Convert 10110111 to Decimal

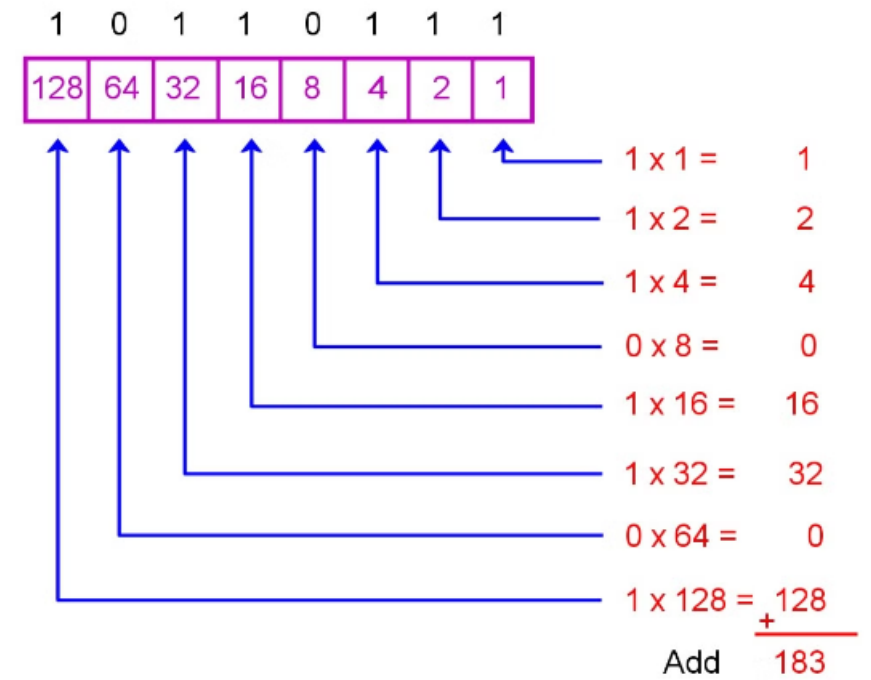

10110111 = 183 decimal

Types of Number System

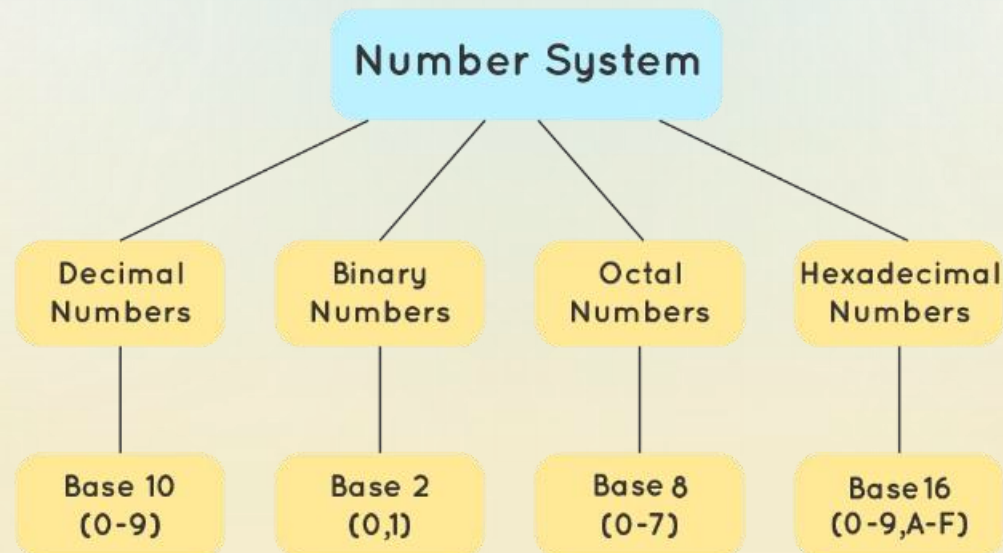

Octal Number System

Octal Basics

The octal number system uses the digits 0 to 7, making it a more compact representation than the binary system.

Conversion to Binary

Each octal digit represents 3 binary digits, allowing easy conversion between octal and binary.

Applications

Octal numbers are commonly used in computer systems and electronics as a shorthand for binary data.

Example

The octal number 257 is equivalent to the binary number 010101111.

Hexadecimal Number System

Hexadecimal Basics

The hexadecimal number system uses 16 digits, 0 to 9 and A to F, to represent numerical values.

Conversion to Binary

Each hexadecimal digit represents 4 binary digits, allowing for compact representation of binary data.

Applications

Hexadecimal numbers are widely used in computer programming, electronics, and digital system design due to their compactness and ease of conversion.

Conversions between Number Number Bases

1

Binary

The fundamental number system used in digital electronics.

2

Octal

A more compact representation of binary data, using 8 digits (0-7).

3

Hexadecimal

A further compact representation using 16 digits (0-9, A-F).

Hexadecimal (base 16)	Decimal (base 10)	Binary (base 2)
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

Practice Problems and Theory Review



Written Exercises

Reinforcing concepts through hands-on problem-solving.



Numerical Conversions

Converting between binary, decimal, octal, and hexadecimal.



Conceptual Questions

Deepening understanding of digital system principles.



Programming Challenges

Applying knowledge to real-world digital system problems.



Complements, Signed Binary Numbers, Binary Code

Complement	Represents the opposite of a number, used for subtraction and negation.
Signed Binary	Allows for the representation of positive and negative numbers using the most significant bit as the sign.
Binary Codes	Encoding schemes that represent information using binary digits, such as ASCII and Gray code.

Binary Storage and Logic

1 Binary Storage


Storing and manipulating binary data in registers and memory.

2 Boolean Logic

Implementing digital logic operations using AND, OR, and NOT gates.

3 Circuit Design

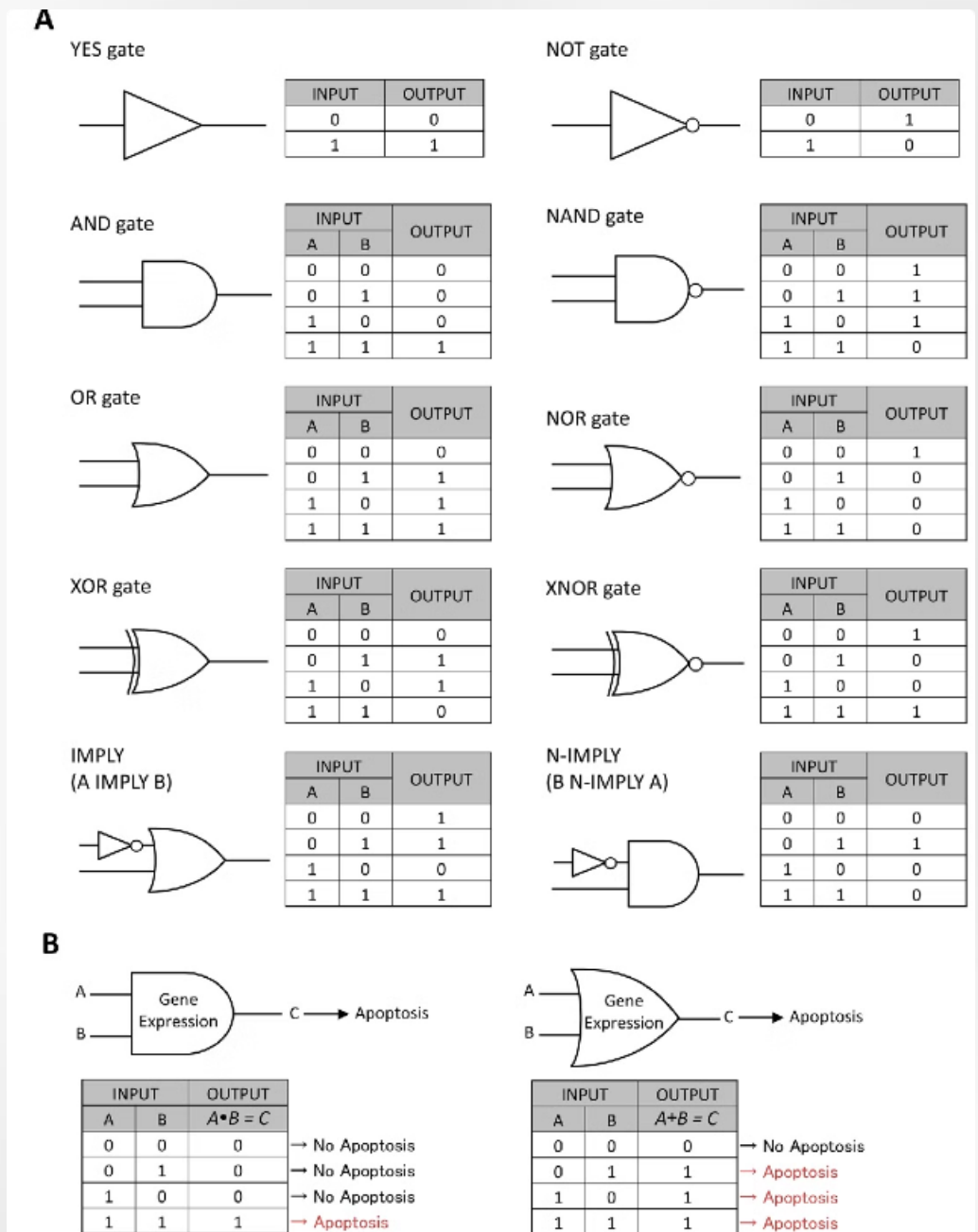Designing and analyzing combinational and sequential digital circuits.



The diagram shows the truth table of Boolean logic operations. When the information is used to design a

Exploring the Fundamentals of Boolean Algebra

Boolean algebra is a mathematical system that deals with the manipulation of logical statements, often represented using binary digits (0 and 1). It forms the foundation for digital electronics and computer programming, enabling efficient data processing and decision-making.



alamy

Image ID: 246RMEP
www.alamy.com

Axiomatic Definition of Boolean Boolean Algebra

1 Basic Axioms





Boolean algebra is defined by a set of fundamental axioms that govern the logical operations of AND, OR, and NOT.

2 Closure Property

The result of any Boolean operation on two or more Boolean variables is also a Boolean variable.

3 Commutativity and Associativity

The order of operands in Boolean operations does not affect the final result.

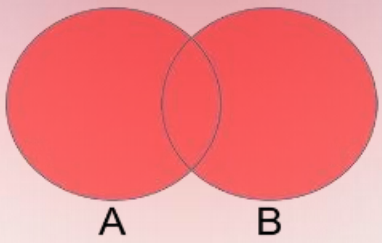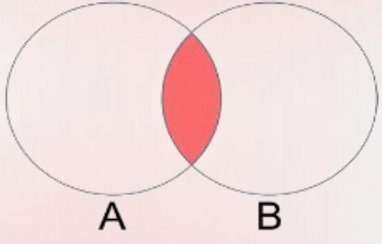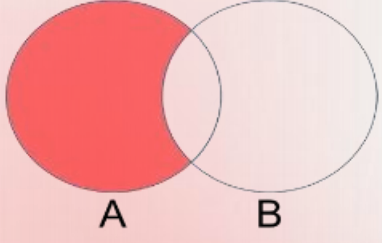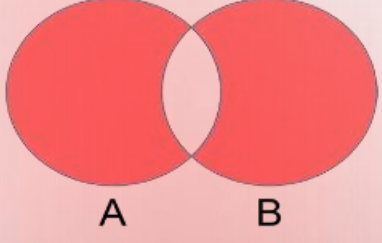Set Operation	Venn Diagram	Interpretation
Union		$A \cup B$, is the set of all values that are a member of A , or B , or both.
Intersection		$A \cap B$, is the set of all values that are members of both A and B .
Difference		$A \setminus B$, is the set of all values of A that are not members of B .
Symmetric Difference		$A \triangle B$, is the set of all values which are in one of the sets, but not both.

Theorems and Properties

Fundamental Theorems


Boolean algebra follows a set of well-established theorems, such as the Commutative, Associative, and Distributive laws.

Algebraic Properties

Boolean variables exhibit properties like idempotency, complementation, and the existence of identity and universal elements.

Duality Principle

 Every theorem or property in Boolean algebra has a dual counterpart, obtained by interchanging AND and OR operations.



Boolean Functions

Definition

A Boolean function is a mapping from a set of Boolean variables to a single Boolean variable, often represented using a truth table.

Functional Completeness

A set of Boolean operations is functionally complete if any Boolean function can be expressed using only those operations.

1

2

3

Canonical Forms

Boolean functions can be expressed in various canonical forms, such as the sum of products (SOP) and product of sums (POS).



Operations on Boolean Functions

Logical Operations

Boolean functions can be combined using the logical operations of AND, OR, and NOT to create more complex expressions.

Complement and Inverse

The complement of a Boolean function is the function that produces the opposite output, while the inverse function reverses the input-output mapping.

Composition and Expansion

Boolean functions can be composed or expanded to create new functions with more variables or simplified expressions.

Transformation Rules

There are various transformation rules, like De Morgan's laws, that can be applied to manipulate Boolean expressions.

Representation of Boolean Functions

1

Truth Tables

Boolean functions can be represented using truth tables, which enumerate all possible input-output combinations.

2


Algebraic Expressions

Boolean functions can also be represented using algebraic expressions, involving the logical operations of AND, OR, and NOT.

3

Karnaugh Maps

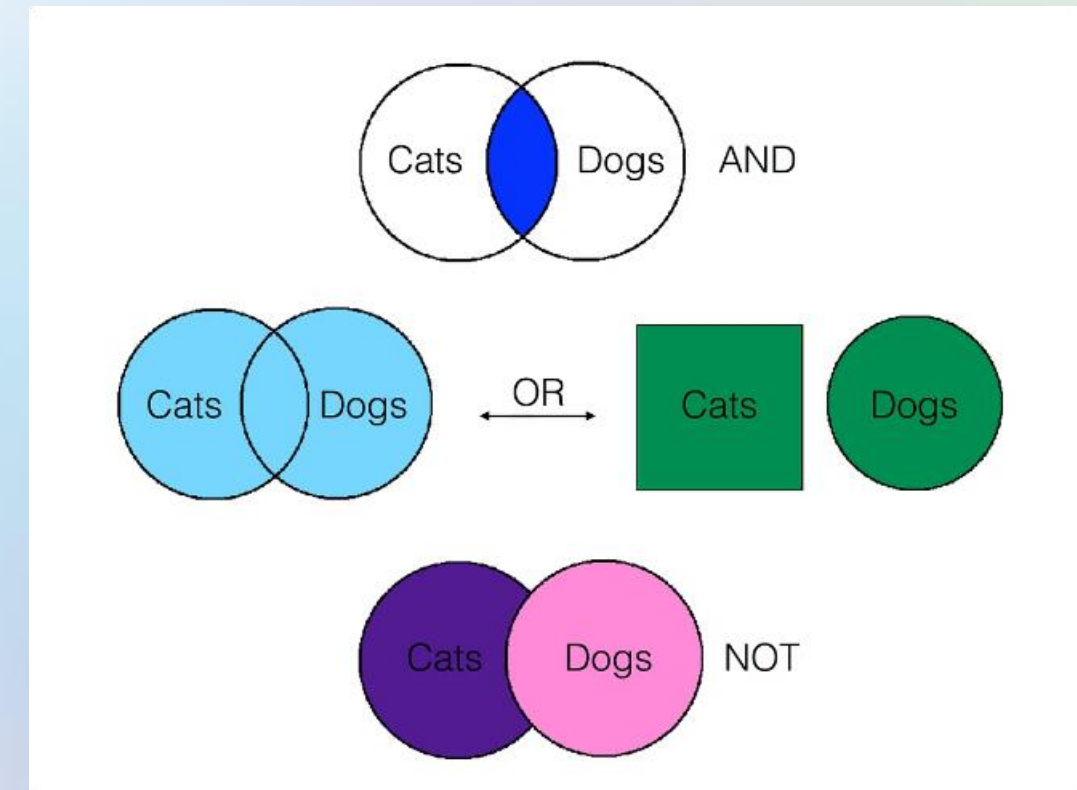Karnaugh maps provide a graphical way to represent and simplify Boolean functions, especially for functions with a small number of variables.



Minimization of Boolean Functions

Finite State Machine Minimization

Advanced

Methods based on triangular table and binate covering

Docsity.com

1

Simplification

Minimizing Boolean functions can lead to more efficient digital circuit designs and reduced computational complexity.

2

Quine-McCluskey Method

The Quine-McCluskey method is a systematic algorithm for finding the minimal sum-of-products form of a Boolean function.

3

Karnaugh Maps

Karnaugh maps can also be used to visually identify and eliminate redundant terms in a Boolean function.

Applications of Boolean Algebra



Digital Electronics

Boolean algebra is the foundation for the design and implementation of digital circuits and logic gates.



Computer Programming

Boolean logic is extensively used in programming languages, algorithms, and data structures to make decisions and manipulate data.




Database Management

Boolean operations are essential for querying and filtering data in database systems, especially in SQL statements.



Artificial Intelligence

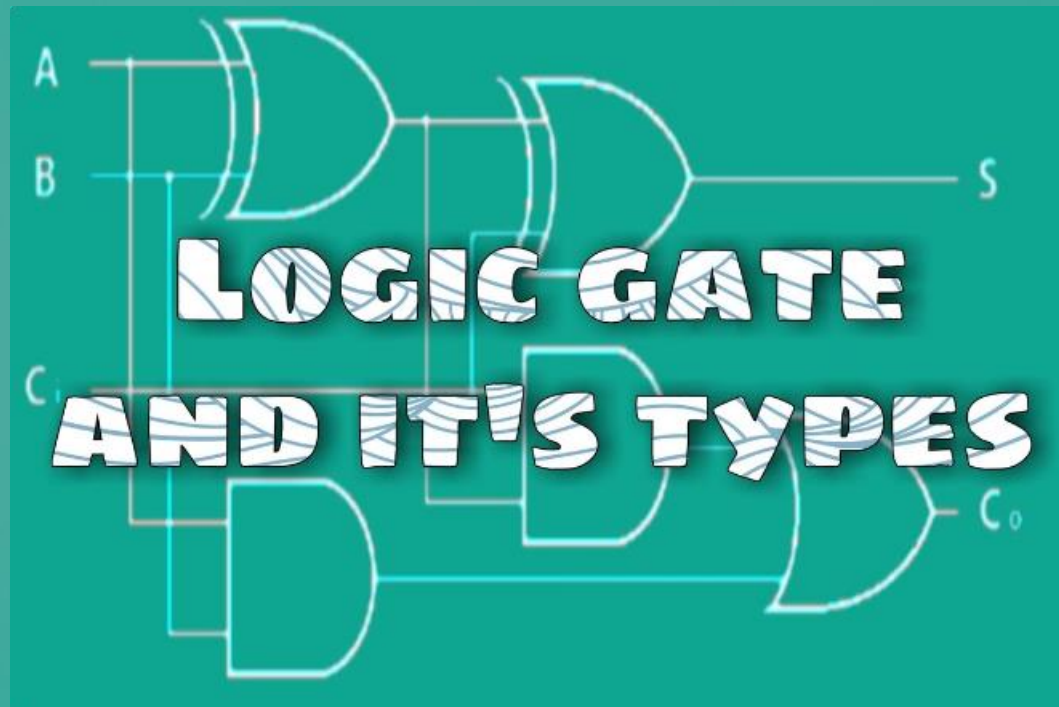



Conclusion

Boolean algebra is a powerful mathematical framework that underpins the fundamental operations of digital systems and computer science. Its principles and properties enable the efficient manipulation and representation of logical information, making it an essential tool for a wide range of applications.

Advanced Topics

Canonical Forms

The standard representations of Boolean functions, such as sum of products (SOP) and product of sums (POS).

Standard Logic Operations


Beyond AND, OR, and NOT, other logical operations like NAND, NOR, and XOR can be defined and used.

Switching Theory

The study of Boolean functions and their applications in the design of digital switching circuits.

Formal Logic Systems

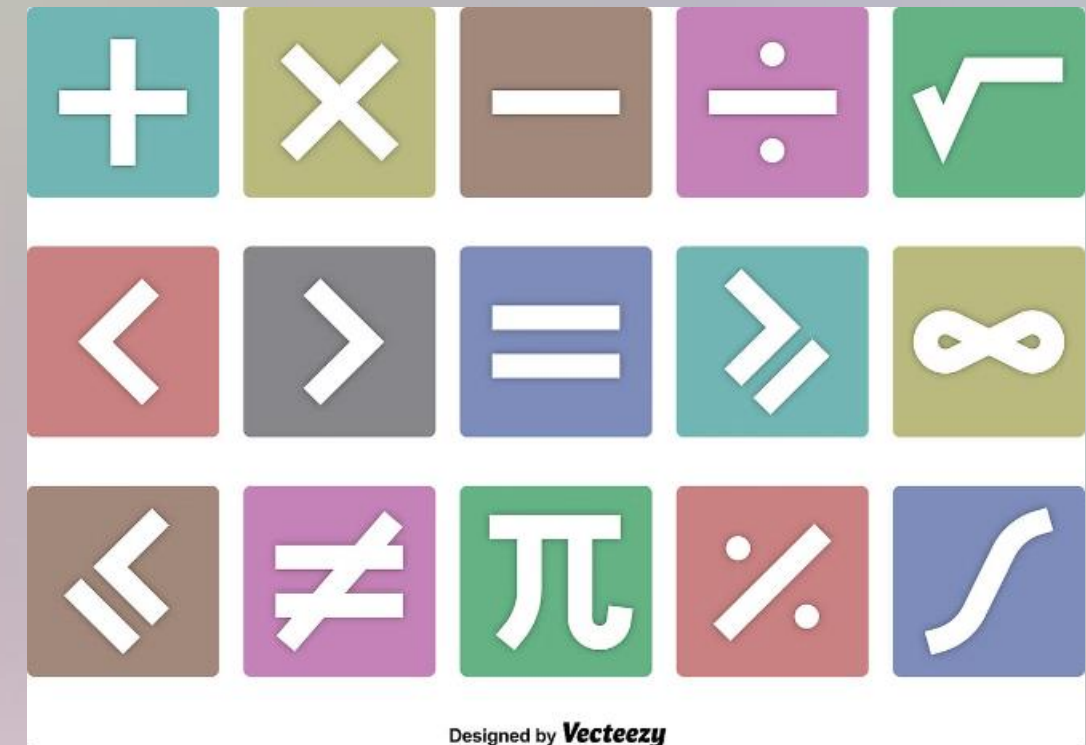The formal mathematical treatment of logical statements and their deductive reasoning, including propositional and predicate logic.



The Map Method: Constructing Karnaugh Maps

F	ab	$\bar{a}\bar{b}$	$\bar{a}b$	$a\bar{b}$	ab
$\bar{c}\bar{d}$	$\bar{a}\bar{b}\bar{c}\bar{d}$ 0000 0	$\bar{a}\bar{b}c\bar{d}$ 1000 8	$\bar{a}b\bar{c}\bar{d}$ 0100 4	$\bar{a}b\bar{c}d$ 1100 12	
$\bar{c}d$	$\bar{a}b\bar{c}\bar{d}$ 0010 2	$\bar{a}b\bar{c}d$ 1010 10	$\bar{a}b\bar{c}d$ 0110 6	$\bar{a}b\bar{c}d$ 1110 14	
$c\bar{d}$	$\bar{a}\bar{b}c\bar{d}$ 0001 1	$\bar{a}\bar{b}cd$ 1001 9	$\bar{a}b\bar{c}d$ 0101 5	$\bar{a}b\bar{c}d$ 1101 13	
cd	$\bar{a}\bar{b}cd$ 0011 3	$\bar{a}\bar{b}cd$ 1011 11	$\bar{a}b\bar{c}d$ 0111 7	$\bar{a}b\bar{c}d$ 1111 15	

Figure 22 electronicclinic.com

1

Step 1

Identify the input variables and their corresponding binary representations.

2

Step 2


Arrange the binary representations in a grid, creating a Karnaugh map.

3

Step 3

Plot the function values (1s and 0s) on the Karnaugh map.

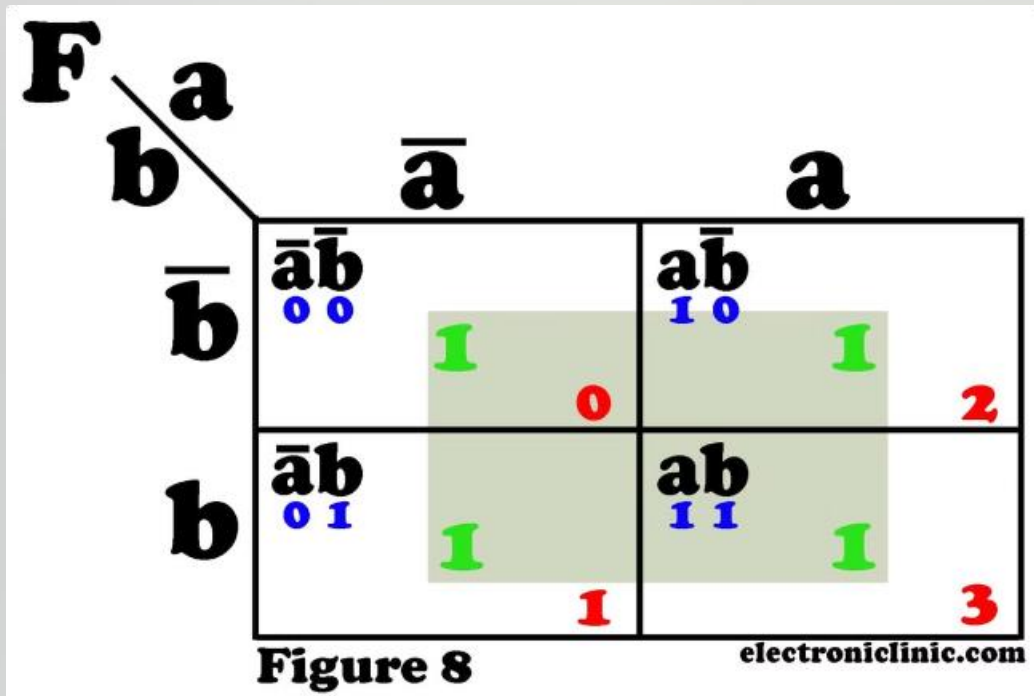Four-Variable Karnaugh Maps: Simplification and Optimization



1

Identify Maximal Groupings

Look for groups of 1s that can be combined to form larger rectangles or squares.

2

Optimize the Boolean Expression

Use the Karnaugh map to simplify the Boolean expression and minimize the number of terms.

3

Handling Don't-Care Conditions

Treat don't-care conditions as 1s to further optimize the Boolean expression.

Five-Variable Karnaugh Maps: Handling Larger Functions

Additional Considerations

Five-variable Karnaugh maps require more complex grouping strategies to identify optimal simplifications.

Techniques

Use techniques like overlapping groups and diagonal adjacency to handle larger functions effectively.

Optimization

The goal is to minimize the number of product terms in the simplified Boolean expression.

Product of Sums Simplification: Techniques and Examples

Identify Maximal Sums

Find the largest sum of literals that can be used to represent the function.

Combine Sums

Combine the maximal sums using the product operation to obtain the simplified expression.

Leverage Don't-Cares

Treat don't-care conditions as 1s to further optimize the product of sums expression.

Verify Simplification

Ensure the simplified expression still accurately represents the original function.

Product of Sums Simplification

	w	x	y	z	F	\bar{F}
0	0	0	0	0	1	0
1	0	0	0	1	1	0
2	0	0	1	0	1	0
3	0	0	1	1	0	1
4	0	1	0	0	1	0
5	0	1	0	1	1	0
6	0	1	1	0	1	0
7	0	1	1	1	0	1
8	1	0	0	0	1	0
9	1	0	0	1	1	0
10	1	0	1	0	0	1
11	1	0	1	1	0	1
12	1	1	0	0	1	0
13	1	1	0	1	1	0
14	1	1	1	0	1	0
15	1	1	1	1	0	1

$F = \bar{y} + \bar{w}z + x\bar{z}$

$\bar{F} = yz + w\bar{x}y$

20 / 50

Don't-Care Conditions: Leveraging Unused Inputs

1

Identify Don't-Cares

Determine the input combinations that are not used or have no defined output.

2

Optimize Expressions

Treat don't-care conditions as 1s to simplify the Boolean expression further.

3

Practical Applications

Don't-care conditions are often used in digital circuit design to reduce hardware complexity.

$$c) A(BC+BC) + AC = A(BC) + AC$$

$$X + X = X$$

$$X=1 \quad 1+1=1$$

NAND and NOR Implementation: Alternate Realizations



NAND Gates

NAND gates can be used to implement any Boolean function by combining multiple NAND gates.




NOR Gates

NOR gates can also be used to implement any Boolean function, providing an alternate realization.



Inverters

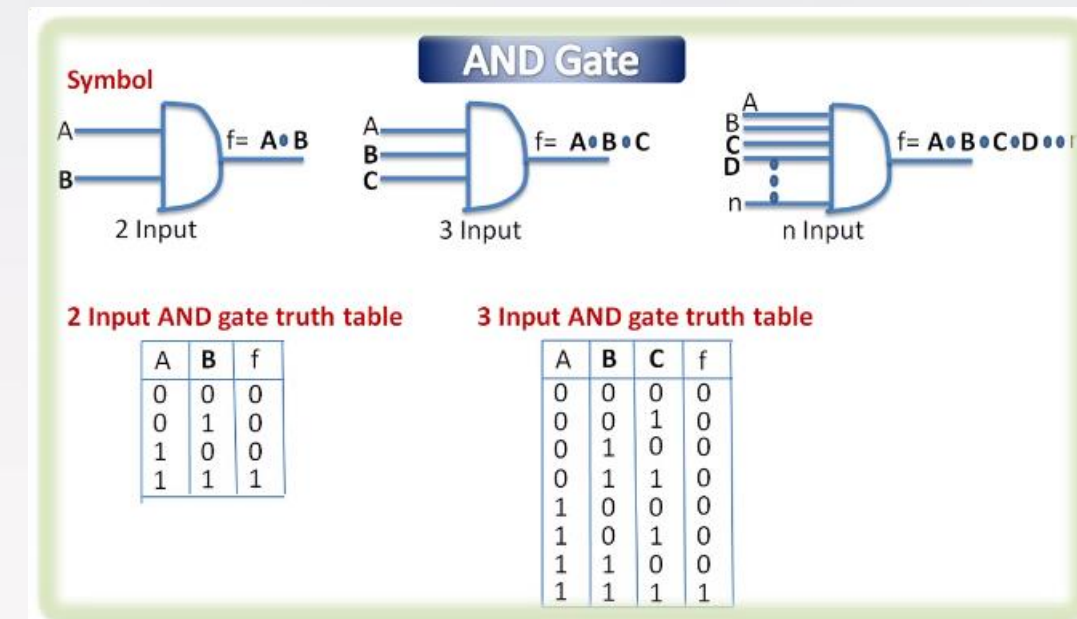
Inverters can be used in combination with NAND or NOR gates to create more complex functions.



Exclusive-OR Function: Representation and Applications

The following logic gate represents:

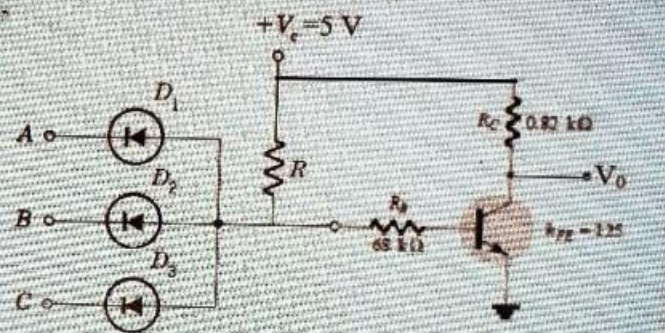- a) Exclusive OR logic gate,
- b) NAND logic gate,
- c) OR logic gate,
- d) Anticoincidence logic gate,
- e) NOR logic gate,
- f) AND logic gate.



Inputs	Output
0 0	0
0 1	1
1 0	1
1 1	0

The exclusive-OR (XOR) function is a fundamental logic operation with various applications, such as in error detection and correction, data encryption, and adder circuits.

Introduction to Combinational Circuits



Combinational circuits are digital logic circuits where the output depends solely on the current input. They combine Boolean logic gates in a complex network to perform various computational tasks, from simple arithmetic to complex decision-making.



Boolean Algebra and Logic Gates

Boolean Algebra

Boolean algebra is the mathematical foundation of combinational circuits, using the operators AND, OR, and NOT to describe logical relationships.

Logic Gates

Logic gates are the building blocks of combinational circuits, implementing the Boolean algebra operations using physical electronic components.

Interconnections

Connecting multiple logic gates in specific arrangements allows for the creation of complex combinational logic circuits.

Truth Tables and Karnaugh Maps

1 Truth Tables

Truth tables systematically list all possible input combinations and the corresponding output values for a combinational circuit.

2 Karnaugh Maps

Karnaugh maps provide a visual tool for simplifying Boolean expressions and minimizing the number of logic gates required.

3 Optimized Design

Analyzing truth tables and Karnaugh maps helps designers create more efficient and cost-effective combinational circuits.

P	Q	$P \vee Q$	$P \rightarrow Q$	$Q \vee P$
T	T	T	T	T
T	F	F	F	T
F	T	F	T	T
F	F	F	T	F

2 Solutions

$A'BCE' + A'BD + A'CDE' + AB'CD' + AC'E + B'CD'E + BC'D + BC'E$

A'BCE'

A'BD

A'CDE'


AB'CD'

AC'E

B'CD'E

BC'D

$$\begin{aligned}
&= C'EE' + C(A'+B)(B+B') && \text{Commutativity} \\
&= C'0 + C(A'+B)(B+B') && \text{Complementarity } C'EE' + C(A'+B)(B+B') \rightarrow C'0 + C(A'+B)(B+B') \\
&= 0C' + C(A'+B)(B+B') && \text{Commutativity} \\
&= 0 + C(A'+B)(B+B') && \text{Null Element theorem } 0C' + C(A'+B)(B+B') \\
&= 0 + C(A'+B)(1) && \text{Complementarity } 0 + C(A'+B)(B+B') \rightarrow 0 + C(A'+B)(1) \\
&= 0 + C(A'+B)1 && \text{Associativity } 0 + C(A'+B)(1) \\
&= 0 + 1C(A'+B) && \text{Commutativity} \\
&= 1C(A'+B) && \text{Identity } 0 + 1C(A'+B) \\
&= C(A'+B) && \text{Identity } 1C(A'+B) \\
&= (CA'+CB) && \text{Distributivity } C(A'+B) \rightarrow (CA'+CB)
\end{aligned}$$

 

Minimization Techniques

Boolean Simplification

Applying Boolean algebra rules and identities to minimize the number of logic gates required.

Karnaugh Map Reduction

Grouping adjacent 1's in a Karnaugh map to identify and eliminate redundant terms.

Quine-McCluskey Method

A systematic algorithm for minimizing Boolean expressions, particularly useful for complex functions.

Analysis Procedure Step-by-Step

Step

1

Identify Inputs and Outputs

Clearly define the circuit's input and output variables to understand the overall functionality.

2


Construct Truth Table

Enumerate all possible input combinations and determine the corresponding output values.


3

Simplify Boolean Expressions

 Apply minimization techniques to optimize the Boolean functions implemented by the circuit.



Combinational Circuit Design Examples

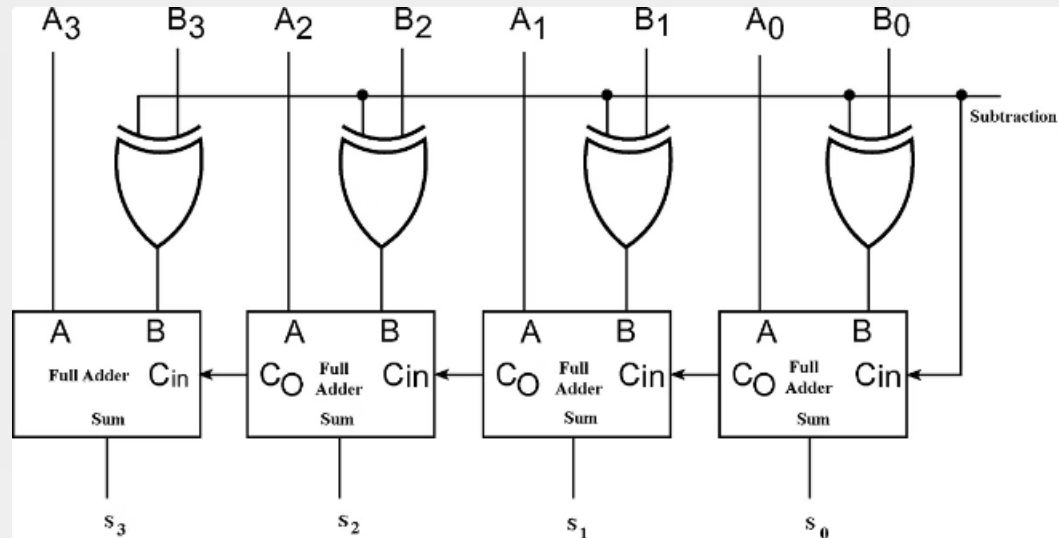

Adder Circuits

Combining full and half adders to perform binary addition operations.



Decoder Circuits

Converting binary inputs into unique output signals for various applications.



Multiplexer Circuits

Selecting one of multiple input signals and routing it to a single output.

Importance of Combinational Circuits

1

Versatility

Combinational circuits can be designed to perform a wide range of digital logic functions.

2

Efficiency

Minimization techniques allow for the creation of compact and cost-effective circuits.

3

Foundations

Combinational logic is the building block for more complex sequential and digital systems.



Conclusion and Key Takeaways

Understand Boolean Algebra

Mastering the fundamental logical operations is crucial for combinational circuit design.

Utilize Optimization Techniques

Applying minimization methods like Karnaugh maps ensures efficient circuit implementation.


Analyze Circuit Behavior

Constructing truth tables and studying circuit functionality is key to successful design.

Explore Combinational Applications

 Combinational circuits have a wide range of uses in digital systems and electronics.





Sequential Circuits: Understanding the Flow of Information Information

Sequential circuits are a fundamental component of digital systems, allowing information to be stored and processed over time. Unlike combinational circuits, sequential circuits have memory elements, enabling them to remember past inputs and produce outputs based on both current and previous inputs.


Latches: The Foundation of Memory


SR Latch

The SR latch is a fundamental memory element that stores a single bit of information. It consists of two cross-coupled NOR gates, where the 'S' input sets the latch to a '1' state and the 'R' input resets it to a '0' state.

D Latch

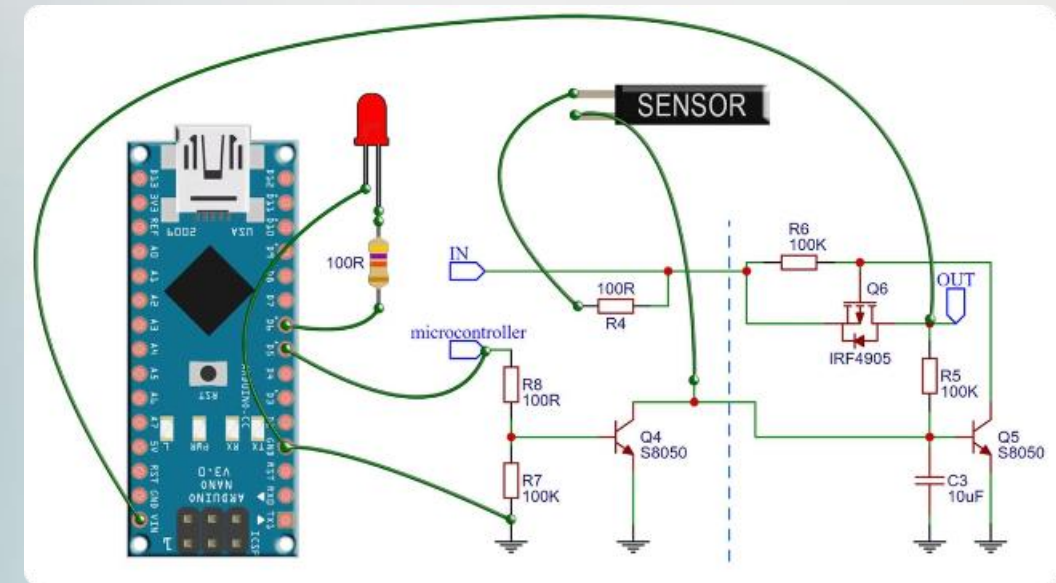The D latch is a variation of the SR latch that uses a single data input (D). The latch stores the value of D when the enable signal is high and maintains its stored value when the enable signal is low.



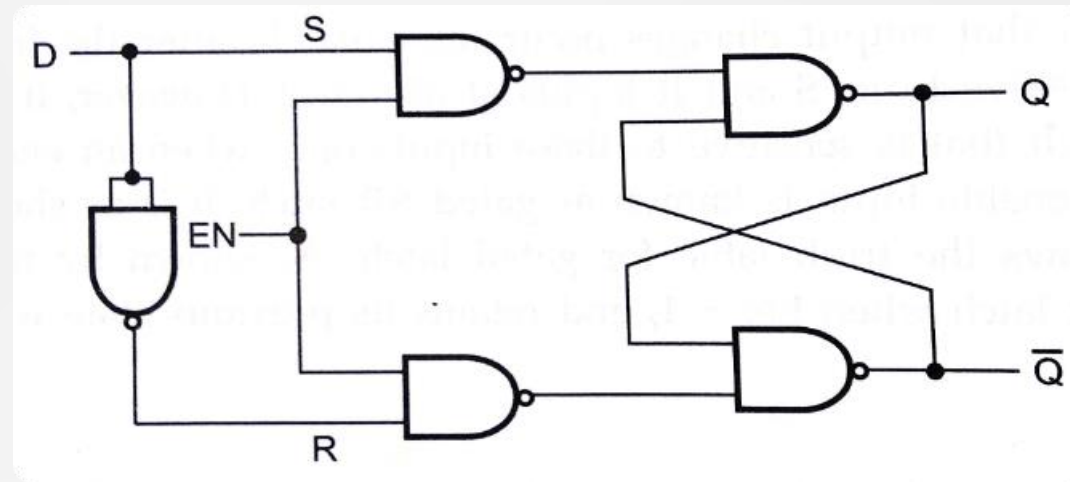

Flip-Flops: The Building Blocks of Sequential Logic

1 SR Flip-Flop

The SR flip-flop is a clocked version of the SR latch, which means it changes its state only when a clock pulse is applied. It is triggered on the rising edge of the clock signal.

2 D Flip-Flop

The D flip-flop is a clocked version of the D latch, providing a more reliable way to store data. It stores the value of D at the rising edge of the clock signal.

3 JK Flip-Flop

The JK flip-flop is a versatile flip-flop that combines the features of the SR and T flip-flops. It allows toggling, setting, and resetting based on the inputs J and K.

Clocked Sequential Circuits: The Heart of Timing

1

Clock Signals

Clock signals are fundamental to clocked sequential circuits. They act as a timing reference for the circuit, controlling when state transitions occur.

2

State Transition

The state of a clocked sequential circuit changes only on the edge of the clock signal. This ensures that all state changes happen synchronously, preventing timing issues.

3

Timing Diagrams

Timing diagrams are visual representations of the signals within a sequential circuit, showing how signals evolve over time.



Timing Diagrams and Waveforms: Understanding Signal Behavior

Pulse Width


The duration of a pulse in a timing diagram, which can be important for understanding the behavior of a circuit.

Edge Detection

Flip-flops are often triggered on specific edges (rising or falling) of the clock signal, which is crucial for synchronization.

Signal Relationships

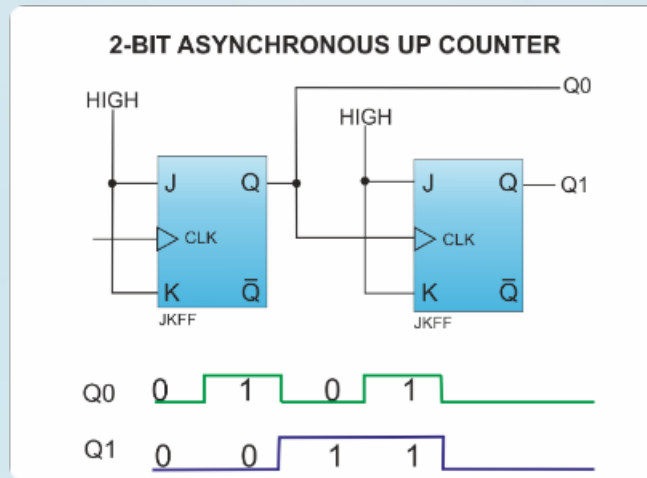Timing diagrams help visualize the relationships between various signals in a circuit, making it easier to analyze and debug the circuit's functionality.



Synchronous and Asynchronous Inputs: The Difference Difference in Timing

Synchronous


Triggered by the clock signal

Changes occur only on the clock edge

Asynchronous

Not triggered by the clock signal

Changes can occur at any time

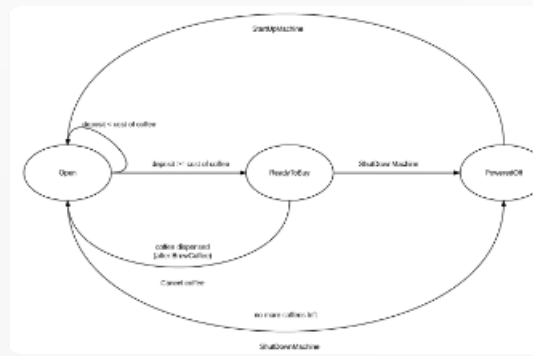

Finite State Machines: The Logic of Sequential Behavior

1

States

A finite state machine (FSM) has a finite number of distinct states that it can be in, representing different memory configurations.

2

Transitions


The FSM transitions between states based on the current state and input signals. These transitions are triggered by the clock signal.

3

Outputs

Each state in an FSM can produce a specific output based on its current state and the received input signals.

 Practical Applications and Design Considerations



Memory Systems

Sequential circuits are essential for implementing memory systems in computers and other digital devices. They are used to store data, such as RAM and ROM.



Timers and Counters

Sequential circuits form the basis of timers and counters used for controlling the timing of events and counting occurrences of signals in digital systems.




Digital Control Systems

They are used in control systems where the output must be based on past inputs and current conditions. This ensures proper response and control based on system history.



Design Considerations

 Key factors include timing analysis, clock signal design, state assignment, and minimizing power consumption. These considerations are crucial for ensuring reliable circuit operation.



State Reduction and Assignment

State reduction and assignment are fundamental concepts in digital design. By simplifying the state space and assigning appropriate binary codes, we can achieve efficient and optimized implementations of digital circuits.

Design Procedure

State Diagram


The first step is to create a state diagram that represents the behavior of the system.

State Reduction

The goal of state reduction is to simplify the state table by eliminating redundant states.

Logic Circuit Design

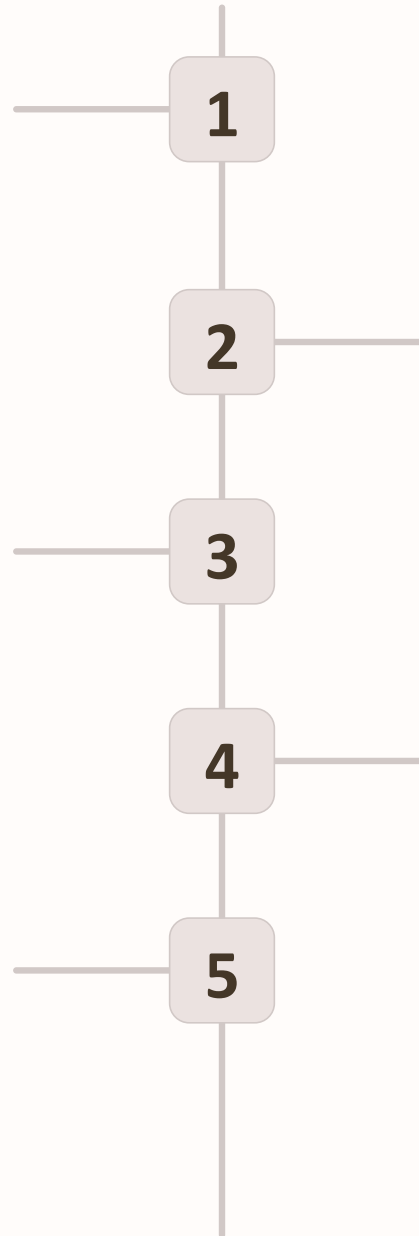Finally, the logic circuit for the system is designed using the assigned binary codes.



State Table

Next, a state table is created, which lists all possible states and the corresponding outputs.

State Assignment

State assignment involves assigning binary codes to each state in the reduced state table.

Registers

1 Storage Elements

Registers are fundamental building blocks in digital systems, acting as memory elements that hold binary data.

3 Clocked Operation


Registers are typically clocked devices, meaning their state changes occur at specific times dictated by a clock signal.

2 Types of Registers

Common types include D-flip flops, JK-flip flops, and T-flip flops, each with unique characteristics and applications.

4 Data Transfer

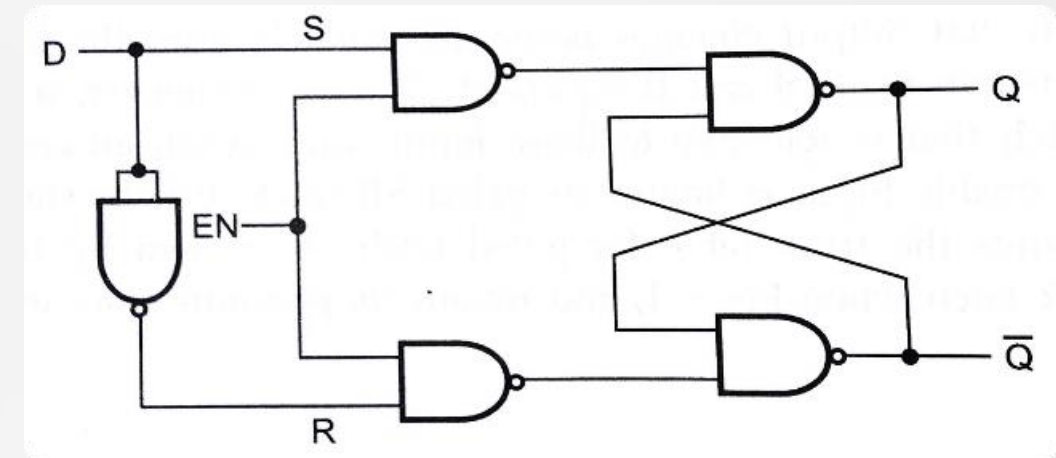Registers allow for the transfer of data between different parts of a digital system, facilitating communication and processing.



Shift Registers

Data Movement

Shift registers are specialized registers that enable the sequential movement of data from one storage element to the next.


Serial-to-Parallel Conversion

Shift registers can convert data from a serial format (one bit at a time) to a parallel format (multiple bits simultaneously).

Applications

They are used in applications like digital communications, data transmission, and signal processing.

Ripple Counters

 

1

Cascaded Flip-Flops

Ripple counters are built using a chain of cascaded flip-flops, where the output of one flip-flop triggers the next.

2

Asynchronous Operation

The output of each flip-flop is delayed, leading to a rippling effect as the counter progresses through its states.

3


Clock Skew

This delay can lead to issues like clock skew, which can affect the accuracy of the counting process.

4

Simple Design

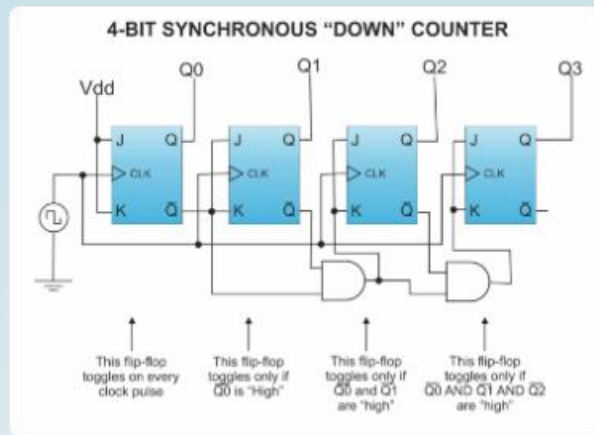Ripple counters are relatively simple to design and implement, making them suitable for basic counting applications.



Synchronous Counters

Feature	Ripple Counter	Synchronous Counter
Clocking	Asynchronous	Synchronous
Timing	Delay between stages	All flip-flops clocked simultaneously
Speed	Slower	Faster
Accuracy	Less accurate	More accurate
Complexity	Simpler	More complex

Other Counters




Up/Down Counters

These counters can count both upwards and downwards, providing flexibility for a wide range of applications.



Decade Counters

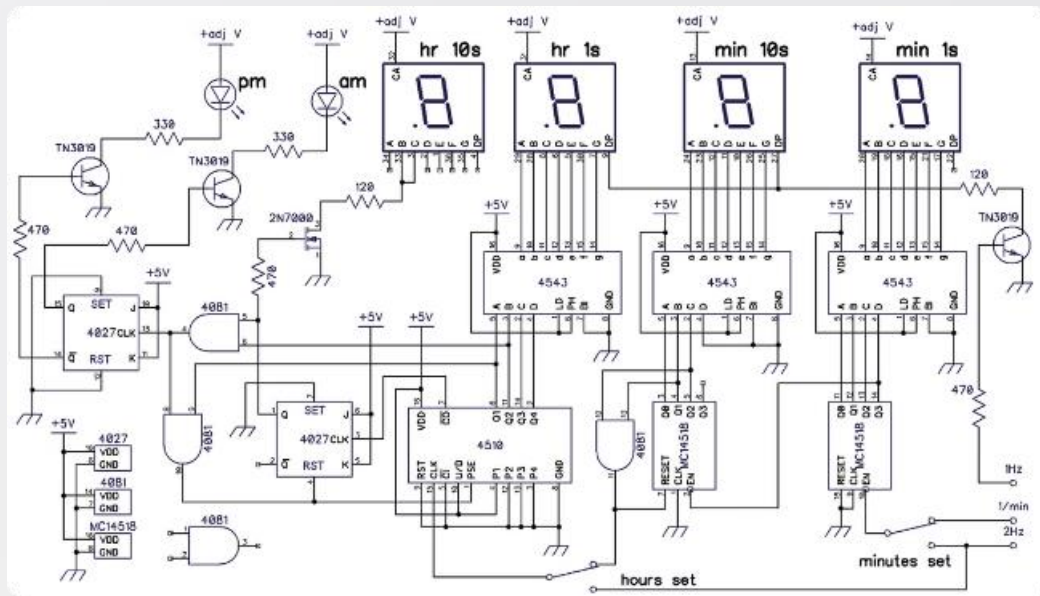Decade counters count in base-10, making them useful for applications that require decimal counting.



Programmable Counters

Programmable counters allow for the modification of their counting sequence, providing greater control and flexibility.




Ring Counters

Ring counters are a type of counter that circulates a single bit through a chain of flip-flops, used for pattern generation and data shifting.

Conclusion

 State reduction, state assignment, and various types of counters are fundamental components of digital design. Understanding these concepts allows for the efficient and reliable implementation of digital circuits that perform a wide range of functions.



Computer Memory

Understanding how computer memory works is crucial for anyone looking to build or troubleshoot a computer system. This presentation will cover the fundamental concepts of computer memory, including different types, functionalities, and their applications.




Random-Access Memory

Dynamic RAM (DRAM)


Dynamic RAM is the most common type of RAM used in computers today. DRAM uses capacitors to store data, which must be refreshed periodically.

Static RAM (SRAM)

 SRAM is a faster and more expensive type of RAM that uses latches to store data. SRAM does not require refreshing, making it ideal for applications where speed is critical.



Memory Decoding

 

1

Address Generation

The CPU generates a physical address that corresponds to the location of the data to be accessed.

2

Address Translation

The address is then translated into a logical address that is used by the memory controller.

3

Memory Access

The memory controller uses the logical address to access the correct memory location and retrieve or store the data.

Error Detection and Correction



1

Parity Bits

Parity bits are used to detect single-bit errors in memory. Parity is calculated for each data byte and stored in an extra bit.

3

Checksums

Checksums are used to verify the integrity of data by calculating a checksum value based on the data.

2

Hamming Codes

Hamming codes are more complex error-detecting and correcting codes that can detect and correct multiple-bit errors.

4

ECC Memory

Error Correction Code (ECC) memory is commonly used in servers and other critical applications where data integrity is essential.

Read-only Memory

Mask ROM

Mask ROM is a type of ROM where the data is permanently stored during the manufacturing process. It is not reprogrammable.

PROM (Programmable ROM)

PROM is a type of ROM that can be programmed once by the user. This process is irreversible.

EPROM (Erasable Programmable ROM)

EPROM is a type of ROM that can be erased by exposing it to ultraviolet light. It can then be reprogrammed.

Programmable Logic Array

AND Gate


Implemented using rows

Programmable by fusing or connecting rows

OR Gate

Implemented using columns

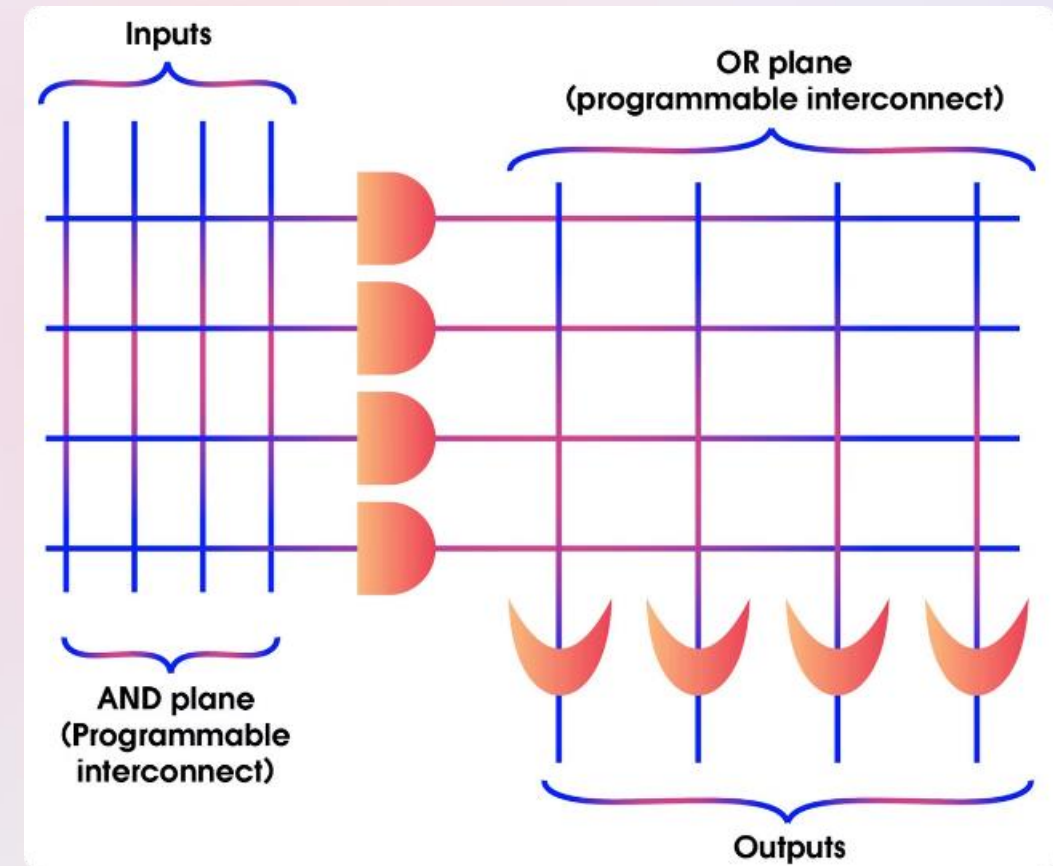Programmable by fusing or connecting columns



Programmable Array Logic

1

AND Plane

The AND plane is used to implement product terms, which are the outputs of the AND gates.

2


OR Plane

The OR plane is used to implement sum terms, which are the outputs of the OR gates.

3

Output Plane

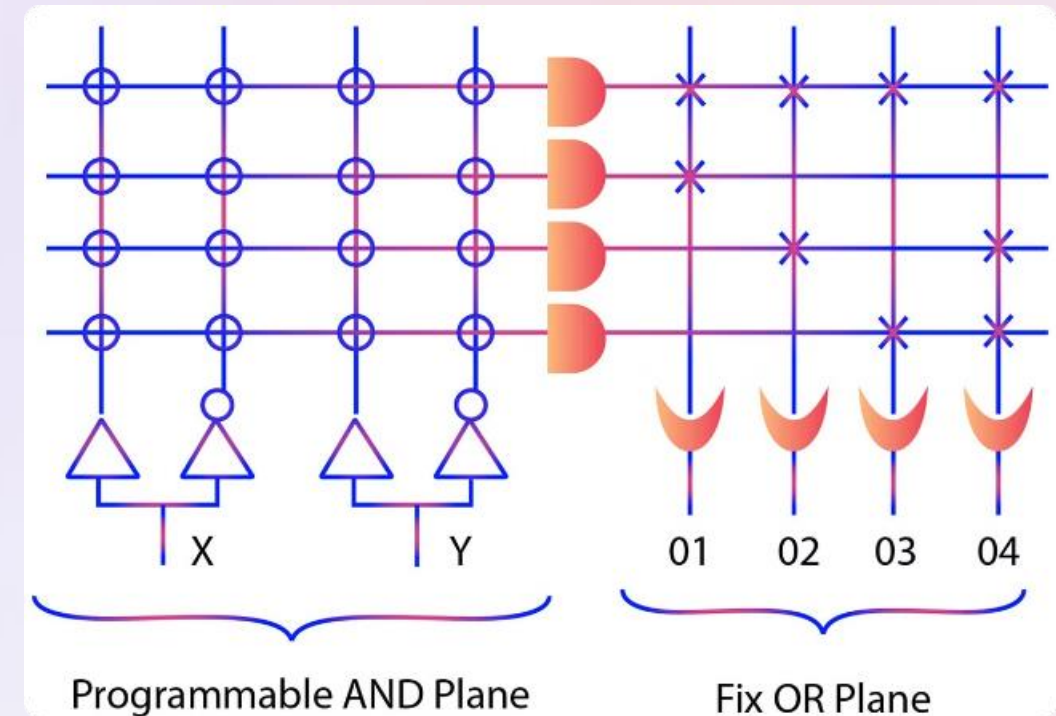The output plane combines the outputs of the OR gates to produce the final output of the PAL.



Sequential Programmable Devices



Flip-Flops

Flip-flops are basic memory elements that store one bit of data. They are used in sequential circuits to implement memory and timing functions.



Shift Registers

Shift registers are sequential circuits that shift data bits from one position to another. They are used in applications such as serial-to-parallel conversion, data storage, and delay lines.




Counters

Counters are sequential circuits that count events. They are used in applications such as timers, frequency dividers, and digital clocks.



State Machines

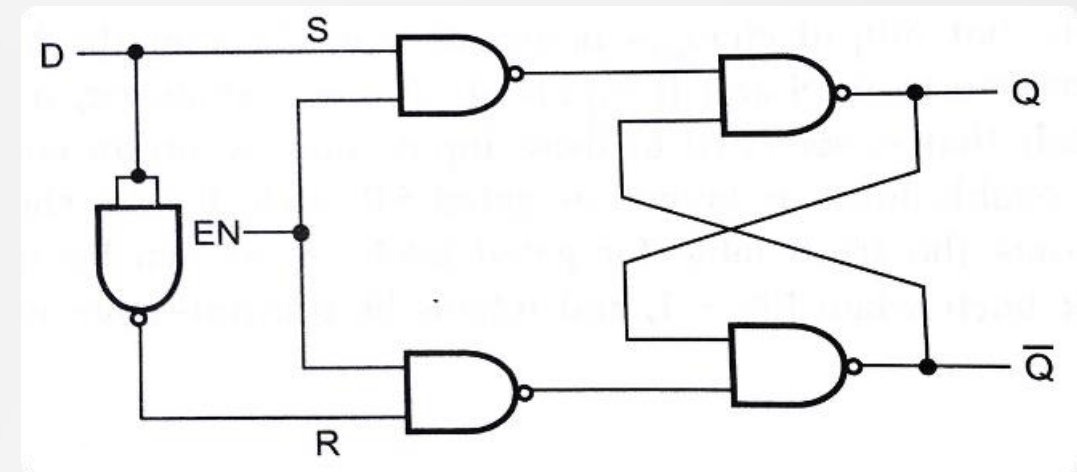
State machines are sequential circuits that have a finite number of states. They are used in applications such as control systems, communication protocols, and game logic.



Sequential Circuits

 Sequential circuits are a fundamental component of digital systems, enabling complex behaviors and memory functions. Understanding their design principles is crucial for building sophisticated electronics.





Analysis Procedure

Step 1: Identify the inputs and outputs

Determine the signals that control the circuit and the signals it produces.

1

Step 3: Draw the state diagram


Visualize the circuit's behavior using a diagram that shows state transitions and output values.

3

2

Step 2: Derive the state table

 Construct a table that maps input combinations to output values for each state.



Circuits with Latches

1

SR Latch

The SR latch is a basic memory element that stores a single bit of data. It has two inputs, Set (S) and Reset (R), and one output, Q.

2

D Latch

A D latch is a variation of the SR latch that uses a single data input (D) to control the output state.

3

JK Latch

The JK latch is a more versatile type of latch that includes both Set and Reset capabilities, allowing for toggling functionality.

Design Procedure

Step 1: Define the problem


Clearly state the functionality of the desired circuit, including its inputs, outputs, and expected behavior.

Step 3: Minimize the state table

Reduce the number of states in the table while preserving the circuit's functionality.

Step 5: Derive the logic equations

 Use Boolean algebra to express the output and next state functions in terms of the inputs and current state.



Step 2: Construct the state table

Represent the circuit's behavior as a table that maps input combinations to output values and state transitions.

Step 4: Assign states to flip-flops

Determine the specific binary code for each state to be stored in the flip-flops.

Step 6: Implement the circuit

Realize the circuit using logic gates, flip-flops, and other necessary components.

Reduction of State and Flow Tables

State Minimization

Reducing the number of states in a state table while preserving functionality simplifies the circuit design and reduces cost.

Flow Table Reduction

A flow table describes the transitions and outputs of a sequential circuit. Reducing its size optimizes the design process.

Race-Free State Assignment

Race Condition

A race condition occurs when multiple state transitions can happen simultaneously, leading to unpredictable outcomes.

Race-Free Assignment

Ensuring that only one flip-flop changes state at a time eliminates race conditions and ensures reliable circuit behavior.



Hazards


Static Hazard

A transient error in the output during a state transition, leading to a momentary incorrect output value.

Dynamic Hazard

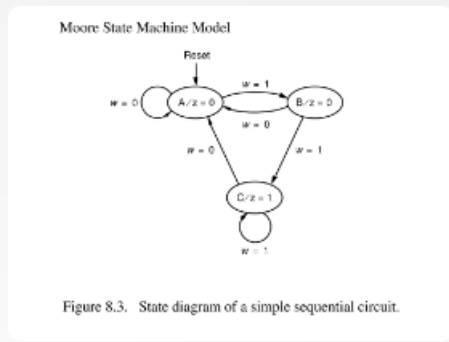Multiple transitions in the output signal during a state change, causing a spike or dip in the output.





Design Example

1

State Table

Define the circuit's behavior with a state table that maps input combinations to output values and state transitions.

2

State Assignment

Assign binary codes to each state to represent them in the flip-flops.

3

Logic Equations

Derive the Boolean equations for the outputs and next state functions.

4

Circuit Implementation

Realize the circuit using logic gates, flip-flops, and other necessary components.