

Code No: 155CB

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech III Year I Semester Examinations, September - 2021****MEASUREMENTS AND INSTRUMENTATION****(Electrical and Electronics Engineering)****Time: 3 Hours****Max. Marks: 75**

**Answer any five questions**  
**All questions carry equal marks**

- - -

- 1.a) By utilizing attracted disc technique explain how electrostatic voltmeter works with help of neat diagram.
- b) A moving coil instrument gives a full-scale deflection of 10mA when the potential difference across its terminal is 100mV. Calculate (i) The shunt resistance for a full-scale deflection corresponding to 100A (ii) The resistance for full-scale reading with 1000V. Calculate the power dissipation in each case. [8+7]
- 2.a) A PMMC ammeter has the following specification Coil dimension are 1cm× 1cm. Spring constant is  $0.15 \times 10^{-6}$  N m / rad, Flux density is  $1.5 \times 10^{-3}$  wb / m. Determine the number of turns required to produce a deflection of 900 when a current 2mA flows through the coil.
- b) Describe the construction and working of PMMC instrument. Derive the equation for deflection if the instruments are spring controlled. [7+8]
3. Differentiate between a C.T. and P.T. Discuss the theory of a P.T with phasor diagrams. Derive the expression for actual transformation ratio, ratio error and phasor angle error of a P.T. [15]
4. Discuss the major sources of errors in the current transformer. What are the means to reduce errors in CT? Explain the design and constructional feature to reduce the error. [15]
5. Explain the construction and working of induction type single-phase energy meter with a neat diagram and derive its equation. [15]
- 6.a) Explain the principle of working of LPF wattmeter.
- b) Explain the operation of a three-phase dynamometer type wattmeter. [7+8]
- 7.a) Describe the circuit of Kelvin double bridge used for measurement of low resistance. Derive the conditions for balance.
- b) Derive an equation for Wien's bridge at balance with a circuit diagram and explain the measurement procedure for measuring unknown frequency using this bridge. [7+8]
- 8.a) How the transducers are classified based on the principle of operation?
- b) Explain the construction and principle of working of an LVDT. [7+8]

R18

Code No: 155CB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, March - 2021

MEASUREMENTS AND INSTRUMENTATION

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Answer any five questions  
All questions carry equal marks

---

- 1.a) A basic d'Arsonval meter movement with an internal resistance,  $R_m = 100\Omega$  and a full scale current of  $I_m = 1mA$  is to be converted in to a multi range D.C. voltmeter with ranges of 0-10V, 0- 50V, 0- 250V,0-500V. Determine the values of various resistances required for potential divider arrangement.
- b) How can you extend the range of Electro static Voltmeters? Elaborate. [8+7]
- 2.a) Compare Polar and Coordinate type AC potentiometers.
- b) Conclude the need of Potential transformer? And list different errors occurred in PTs. [8+7]
- 3.a) How can you test energy meter by phantom loading? Explain.
- b) Explain the construction and working of three element dynamometer wattmeter. [7+8]
- 4.a) How could you measure medium resistance using bridge? Elaborate.
- b) Construct the circuit Maxwell's bridge and develop relation for unknown inductance. [8+7]
- 5.a) Explain the principle of operation of Thermocouple and mention its advantages.
- b) Discuss principle of operation of Capacitance transducers and list their applications. [8+7]
- 6.a) Explain the Principle and working of DC potentiometer with a neat sketch.
- b) Explain the working principle of repulsion type moving iron instrument. [7+8]
- 7.a) Prove that for electrodynamic type wattmeter  
True power =  $\{\cos \Phi / [\cos \Phi \cos (\Phi - \beta)]\}$  x actual wattmeter reading  
Where  $\cos \Phi$  = power factor of the circuit  
 $\beta = \tan^{-1} (\omega L/R)$  where L and R are the inductance and resistance of the pressure coil of the circuit.
- b) How could you measure frequency using Wein's bridge? Discuss with the help of diagram. [8+7]
- 8.a) Discuss principle of operation of True RMS meters.
- b) Categorize the errors occurred in instrument transformers and describe them. [7+8]

---ooOoo---

Code No: 155CB

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech III Year I Semester Examinations, January/February - 2023****MEASUREMENTS AND INSTRUMENTATION****(Electrical and Electronics Engineering)****Time: 3 Hours****Max. Marks: 75**

- Note:** i) Question paper consists of Part A, Part B.  
ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.  
iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART – A****(25 Marks)**

- 1.a) Define controlling torque and deflecting torque. [2]
- b) Draw sketches for range extension of ammeter and voltmeter. [3]
- c) What are instrument transformers? What are their uses? [2]
- d) Define ratio error and phase angle error in potential transformer. [3]
- e) What is tri-vector meter? What are its applications? [2]
- f) Define driving and braking torques of induction type energy meter. [3]
- g) State the conditions for AC bridge balancing. [2]
- h) Draw the circuit diagram for H. V. Schering Bridge and write its uses. [3]
- i) What are true RMS meters and what are their applications? [2]
- j) Write the working principle of strain gauge and define its gauge factor. [3]

**PART – B****(50 Marks)**

- 2.a) Explain the principle and working of PMMC type instruments and derive the expressions for its deflecting and controlling torque.
- b) Explain with a neat sketch the working of attracting disc type electrostatic volt meter and describe the range extension of E.S. Volt meter. [5+5]

**OR**

- 3.a) Explain the principle and working of electrometer type volt meter and describe their range extension.
- b) A deflecting electrostatic voltmeter gives full scale deflection of 40 degrees with 9V applied to its terminals. Its capacitance is 10pF at zero deflection and 30 pF at 30° and varies uniformly with deflection. The moment of inertia of moving vanes is  $0.02 \times 10^{-6} \text{ kg/m}^2$ . Calculate the undamped period of instrument. [5+5]

- 4.a) Describe the principle and operation of D. C. Crompton's potentiometer with a neat diagram and explain how unknown resistance and voltage is measured using it.
- b) Derive the expressions for the phase angle errors of a current transformer with a neat phasor diagram. [5+5]

**OR**

- 5.a) Explain the principle and working of A.C. Potentiometer with a neat diagram and describe its standardization.
- b) Explain the construction, principle and working of current transformer. Explain the Wilson compensation method for reduction of errors in current transformers. [5+5]

- 6.a) Explain the construction, principle and operation of single phase three element electro dynamometer type watt meter and derive its torque equation.
- b) If the reactance of the pressure coil circuit of a watt meter is 1 percent of its resistance, calculate the percentage error due to this cause at power factors of 0.8, 0.5 and 0.1 respectively. [6+4]

**OR**

- 7.a) Explain with neat sketches the measurement of active and reactive powers in balanced and unbalanced systems.
- b) Explain the extension of ranges of watt meters using instrument transformers with help of neat diagrams. [6+4]
- 8.a) Draw the neat sketch of Kelvin's double bridge for measurement of low resistance and describe its working.
- b) Explain with a neat circuit the working of Wein's bridge for measurement of capacitance and frequency of the supply voltage and derive the expression for unknown capacitance and frequency. [5+5]

**OR**

- 9.a) Describe the working of Maxwell's inductance capacitance bridge for measurement of unknown inductance and derive the expression for its balance condition. Draw its phasor diagram.
- b) Explain with neat diagram for measurement of capacitance and loss angle using Desauty's Bridge. [5+5]
- 10.a) Explain the classification of transducers with examples and discuss the general characteristics of transducers.
- b) Describe with a neat sketch the principle and working of piezoelectric accelerometer and derive the expression for its output. [5+5]

**OR**

- 11.a) Explain the construction, working principle and applications of capacitive transducers.
- b) Explain the methods of measurement of torque on rotating shafts using strain gauges with help of neat sketches. [5+5]

Code No: 155CB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, February - 2022

MEASUREMENTS AND INSTRUMENTATION

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions  
All questions carry equal marks

- - -

- 1.a) A moving coil instrument gives a full-scale deflection of 10mA when the potential difference across its terminal is 100mV. Calculate,  
i) The shunt resistance for a full-scale deflection of 100A  
ii) Find the resistance for full-scale reading with 100V  
Also, calculate the power dissipation in each case.  
b) Derive an equation for the torque developed in PMMC instrument. [8+7]
- 2.a) A PMMC ammeter has following specification, coil dimension of 1cm×1cm, spring constant is  $0.15 \times 10^{-6}$  N-m/rad, Flux density is  $1.5 \times 10^{-3}$  wb/m<sup>2</sup>. Determine the number of turns required to produce a deflection of 90°, when a current of 2mA flows through the coil.  
b) With the help of a neat diagram, explain the working of attracted disc type voltmeter. [7+8]
- 3.a) Discuss how AC potentiometer can be used for calibration of wattmeter.  
b) Explain the procedure to calibrate voltmeter and ammeter using DC potentiometer. [8+7]
- 4.a) With help of a neat diagram explain the working of coordinate type potentiometer.  
b) Draw the equivalent circuit diagram and phasor diagram of the current transformer. [8+7]
- 5.a) Discuss the construction and Working Principle of Electrodynamic type 1-φ wattmeter with help of a neat diagram.  
b) Explain any two errors that occur in electrodynamic type 1-φ wattmeter and its compensation. [9+6]
- 6.a) With help of a neat diagram, explain the construction and working of a three-phase energy meter.  
b) Two-watt meters are connected to measure the input to a balanced 3 phase circuit indicating 2000W and 500W respectively. Find the power factor of a circuit,  
i) When both the reading is positive and  
ii) When the latter reading is obtained after reversing the connections to the current coil of the first instrument. [9+6]

- 7.a) Draw the circuit of Kelvin double bridge used for measurement of low resistance. Explain its working principle
- b) An AC bridge is balanced at 2KHz with the following components in each arm: Arm AB=10K $\Omega$ , Arm BC=100 $\mu$ F in series with 100K $\Omega$ , Arm AD=50K $\Omega$ . Find the unknown impedance  $R \pm jX$  in the arm DC, if the detector is between BD. [8+7]
- 8.a) Derive an equation for gauge factor in strain gauge.
- b) With help of a neat diagram, explain the principle and working of LVDT. [7+8]

---ooOoo---

used paper feb-22 jntu

**Code No: 155CB****JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech III Year I Semester Examinations, August - 2022****MEASUREMENTS AND INSTRUMENTATION****(Electrical and Electronics Engineering)****Time: 3 Hours****Max. Marks: 75**

**Answer any five questions**  
**All questions carry equal marks**

- - -

- 1.a) Derive the equation for deflection if the instruments are spring controlled. In PMMC instrument.
- b) Explain the working of M. I. instrument. [8+7]
- 2.a) By utilizing Quadrant method briefly explain the working of electrostatic voltmeter with neat diagram.
- b) A moving coil instrument gives a full-scale deflection of 10mA when the potential difference across its terminal is 100mV. Calculate (i) The shunt resistance for a full-scale deflection corresponding to 100A (ii) The resistance for full-scale reading with 1000V. Calculate the power dissipation in each case. [8+7]
- 3.a) With help of a neat diagram explain the working of Crompton type DC potentiometer.
- b) Enumerate the steps used in standardization of DC potentiometer. [8+7]
- 4.a) Compare C. T with P. T.
- b) Derive the expression for ratio error of a C. T. [6+9]
- 5.a) Explain the construction, working principle of a three-phase wattmeter. What is the importance of deflecting torque in these analog instruments?
- b) Derive the torque equation for an electro-dynamometer type of wattmeter. [8+7]
- 6.a) With help of a neat diagram explain the working of Single phase induction type energy meter.
- b) Briefly discuss about the working of LPF wattmeter with help of a neat diagram. [8+7]
- 7.a) Derive the bridge balance condition for the Maxwell bridge and Schering bridge.
- b) Derive an equation for measurement of low resistance using Kelvin double bridge. [8+7]
- 8.a) Describe the principle of working and circuit diagram of a digital storage oscilloscope with help of a neat diagram.
- b) Explain the working of photo voltaic cell and photoconductive cells with suitable diagram. [8+7]