

BEE OLD QUESTION PAPERS

Q.P Code: EE1104ES Hall Ticket No.

NARSIMHAREDDY ENGINEERING COLLEGE (UGC AUTONOMOUS)

I B.Tech I Semester (NR21) Supplementary Examination, January/February 2024
BASIC ELECTRICAL ENGINEERING
(Common to ECE, CSE (CS), CSE (AI&ML), CSE (DS))

Time : 3 hours Maximum marks: 70


- Note:
- This question paper contains two parts, A and B
 - Part A is compulsory which carries 20 marks (10 sub questions are two from each unit carry 2 Marks). Answer all questions in Part A
 - Part B Consists of 5 Units. Answer one question from each unit. Each question carries 10 Marks and may have a, b sub questions

Part-A (20 Marks)
Answer all questions

Q.No	Question	M	CO	BL
1) a	State Kirchhoff's current law.	2	CO1	L1
b	What are the limitations of Ohm's law?	2	CO1	L1
c	Define real power and reactive power	2	CO2	L2
d	What is resonance?	2	CO2	L1
e	What is auto transformer?	2	CO3	L1
f	What is hysteresis loss in transformer?	2	CO3	L1
g	Define voltage regulation of alternator.	2	CO4	L1
h	Draw the equivalent circuit of induction motor	2	CO4	L2
i	Why fuse is used in a circuit?	2	CO5	L1
j	What is the main objective of earthing?	2	CO5	L1

Part-B (50 Marks)
Answer all the Units
All Questions carry equal Marks

Q.No	Question	M	CO	BL
UNIT-I				
2) a	State and explain Thevenin's theorem?	5	CO1	L2
b	Discuss resistor, inductor, capacitor with relevant expression?	5	CO1	L3
OR				
3) a	Write about difference between Voltage source & Current source?	5	CO1	L2
b	Using the Thevenin's theorem calculate the current in 5ohm resistor?	5	CO1	L3

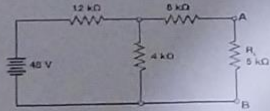

Page 2 of 2

UNIT-II				
4) a	A voltage of 50v with 50HZ frequency is applied to a series RLC circuit with R=100 ohm, L=0.5H and C=40microfarad. Determine i) impedance ii) current iii) power factor iv) phase angle between voltage and current	5	CO2	L4
b	Explain behavior of series RLC circuit?	5	CO2	L3
OR				
5) a	Explain about series RC circuit and derive expression for voltage, current, power and draw phasor diagram.	5	CO2	L3
b	A current of 250 mA flows through a perfect inductor, when it is connected to a 5khz supply. Determine the inductance value	5	CO2	L2
UNIT-III				
6) a	Derive EMF Equation Of Single Phase Transformer?	5	CO3	L3
b	A 125 KVA transformer having primary voltage of 2000V at 50 Hz has 182 primary and 40 secondary turns. Neglecting losses, Calculate (i)The full load primary and secondary currents.(ii)The no load secondary induced EMF (iii)Maximum flux in the core	5	CO3	L3
OR				
7) a	Obtain Conditions For Maximum Efficiency of a Single-Phase Transformer?	5	CO3	L3
b	Explain Losses in Single Phase Transformer?	5	CO3	L3
UNIT-IV				
8) a	State starting methods of three phase induction motor and explain any of them in details.	5	CO4	L2
b	Derive the EMF equation for the alternator?	5	CO4	L3
OR				
9) a	Explain the construction, working principle of single phase Induction motor	5	CO4	L3
b	Explain speed control of induction motor	5	CO4	L2
UNIT-V				
10) a	Compare MCB with MCCB?	5	CO5	L2
b	A consumer uses 10 KW geyzer, 6 KW electric furnace & five 100 W bulbs for 15 hours. How many units (KWhr) of electrical energy have been used?	5	CO5	L3
OR				
11) a	What are the different types of wires and cables? Explain	5	CO5	L2
b	State various types of batteries and their applications?	5	CO5	L3

--0000--

Page 2 of 2

Q.P Code: EE1104ES Hall Ticket No.

NARSIMHAREDDY ENGINEERING COLLEGE (UGC AUTONOMOUS)

I B.Tech I Semester (NR21) Supplementary Examination, January/February 2024
BASIC ELECTRICAL ENGINEERING
(Common to ECE, CSE (CS), CSE (AI&ML), CSE (DS))

Time : 3 hours Maximum marks: 70


- Note:
- This question paper contains two parts, A and B
 - Part A is compulsory which carries 20 marks (10 sub questions are two from each unit carry 2 Marks). Answer all questions in Part A
 - Part B Consists of 5 Units. Answer one question from each unit. Each question carries 10 Marks and may have a, b sub questions

Part-A (20 Marks)
Answer all questions

Q.No	Question	M	CO	BL
1) a	State Kirchhoff's current law.	2	CO1	L1
b	What are the limitations of Ohm's law?	2	CO1	L1
c	Define real power and reactive power	2	CO2	L2
d	What is resonance?	2	CO2	L1
e	What is auto transformer?	2	CO3	L1
f	What is hysteresis loss in transformer?	2	CO3	L1
g	Define voltage regulation of alternator.	2	CO4	L1
h	Draw the equivalent circuit of induction motor	2	CO4	L2
i	Why fuse is used in a circuit?	2	CO5	L1
j	What is the main objective of earthing?	2	CO5	L1

Part-B (50 Marks)
Answer all the Units
All Questions carry equal Marks

Q.No	Question	M	CO	BL
UNIT-I				
2) a	State and explain Thevenin's theorem?	5	CO1	L2
b	Discuss resistor, inductor, capacitor with relevant expression?	5	CO1	L3
OR				
3) a	Write about difference between Voltage source & Current source?	5	CO1	L2
b	Using the Thevenin's theorem calculate the current in 5ohm resistor?	5	CO1	L3

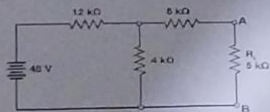

Page 2 of 2

UNIT-II				
4) a	A voltage of 50v with 50HZ frequency is applied to a series RLC circuit with R=100 ohm, L=0.5H and C=40microfarad. Determine i) impedance ii) current iii) power factor iv) phase angle between voltage and current	5	CO2	L4
b	Explain behavior of series RLC circuit?	5	CO2	L3
OR				
5) a	Explain about series RC circuit and derive expression for voltage, current, power and draw phasor diagram.	5	CO2	L3
b	A current of 250 mA flows through a perfect inductor, when it is connected to a 5khz supply. Determine the inductance value	5	CO2	L2
UNIT-III				
6) a	Derive EMF Equation Of Single Phase Transformer?	5	CO3	L3
b	A 125 KVA transformer having primary voltage of 2000V at 50 Hz has 182 primary and 40 secondary turns. Neglecting losses, Calculate (i)The full load primary and secondary currents.(ii)The no load secondary induced EMF (iii)Maximum flux in the core	5	CO3	L3
OR				
7) a	Obtain Conditions For Maximum Efficiency of a Single-Phase Transformer?	5	CO3	L3
b	Explain Losses in Single Phase Transformer?	5	CO3	L3
UNIT-IV				
8) a	State starting methods of three phase induction motor and explain any of them in details.	5	CO4	L2
b	Derive the EMF equation for the alternator?	5	CO4	L3
OR				
9) a	Explain the construction, working principle of single phase Induction motor	5	CO4	L3
b	Explain speed control of induction motor	5	CO4	L2
UNIT-V				
10) a	Compare MCB with MCCB?	5	CO5	L2
b	A consumer uses 10 KW geyzer, 6 KW electric furnace & five 100 W bulbs for 15 hours. How many units (KWhr) of electrical energy have been used?	5	CO5	L3
OR				
11) a	What are the different types of wires and cables? Explain	5	CO5	L2
b	State various types of batteries and their applications?	5	CO5	L3

--0000--

Page 2 of 2

Code No: 181AB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech I Year I Semester Examinations, March/April - 2023

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT, CSIT, CE(SE), CSE(CS), CSE(DS), CSD)

Time: 3 Hours

Max. Marks: 60

Note: This question paper contains two parts A and B.

i) Part- A for 10 marks, ii) Part - B for 50 marks.

- Part-A is a compulsory question which consists of ten sub-questions from all units carrying equal marks.
- Part-B consists of ten questions (numbered from 2 to 11) carrying 10 marks each. From each unit, there are two questions and the student should answer one of them. Hence, the student should answer five questions from Part-B.

PART- A


(10 Marks)

- What is ideal voltage source? [1]
- Define KVL. [1]
- What is active power? [1]
- Define average value of sinusoidal quantity? [1]
- What is a step up Transformer? [1]
- Define regulation of a transformer. [1]
- What type of material is used for brushes of a d.c machine? [1]
- How many windings are present at the time of starting a single phase Induction motor? [1]
- What is the full form of M.C.C.B? [1]
- What is the energy consumed by 1000 watts heater in 3 hours? [1]

PART-B

(50 Marks)

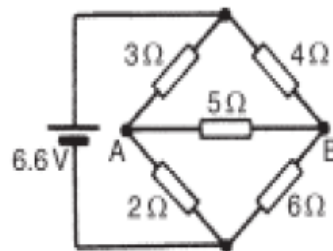- State and explain Thevenin's theorem.
- For the bridge network shown in figure below, find the current in the 5 resistor, and its direction, by using Thevenin's theorem. [5+5]



OR

- 3.a) Derive an expression for transient current in R-L series circuit excited by a d.c source.
 b) Explain the V-I relation of R, L and C elements. [6+4]

4. The following table gives the corresponding values of current and time for a half cycle of alternating current.

Time t (msec)	0	0.5	1.0	1.5	2.0	2.5	3.0	3.5	4.0	4.5	5.0
Current i (A)	0	7	14	23	40	56	68	76	60	5	0

Assuming the negative half cycle is identical in shape to the positive half cycle, plot the waveform and find (a) the frequency of the supply, (b) the instantaneous values of current after 1.25 ms and 3.8 ms, (c) the peak or maximum value, (d) the mean or average value, and (e) the r.m.s value of the waveform. [10]

OR

- 5.a) Derive an expression for resonance frequency of R-L-C series circuit connected to an alternating supply of variable frequency.
 b) A coil has an inductance of 40 mH and negligible resistance. Calculate its inductive reactance and the resulting current if connected to a 240 V, 50 Hz supply. [6+4]
- 6.a) Derive an e.m.f equation of a single phase transformer.
 b) A 4500 V/225 V, 50 Hz single-phase transformer is to have an approximate e.m.f. per turn of 15 V and operate with a maximum flux of 1.4 T. Calculate (i) the number of primary and secondary turns and (ii) the cross-sectional area of the core. [6+4]

OR

- 7.a) What is an Auto transformer? Give its advantages and state its applications.
 b) What are the advantages of 3-phase transformers? Draw various schemes of 3-phase transformer connections. [5+5]
- 8.a) Explain the constructional details of a d.c machine. Explain the working of a d.c generator.
 b) Draw the various characteristics of a d.c shunt motor. [6+4]

OR

- 9.a) Explain the working of a 3-phase Induction motor with a neat sketch.
 b) The stator of a 3-phase, 4-pole induction motor is connected to a 50 Hz supply. The rotor runs at 1455 rev/min at full load. Determine (i) the synchronous speed and (ii) the slip at full load. [6+4]
- 10.a) Explain the working of (i) SFU (Switch Fuse Unit) (ii) ELCB.
 b) What are the advantages of improving the power factor of a system? [6+4]

OR

- 11.a) What are the differences between primary cells and secondary batteries?
 b) Explain different types of wires used in domestic as well as commercial buildings. [4+6]

Code No: 151AG

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech I Year I Semester Examinations, June - 2022

BASIC ELECTRICAL ENGINEERING

(Common to EEE, CSE, IT, CSIT, ITE, CE(SE), CSE(CS), CSE(DS), CSE(Networks), CSED)

Time: 3 Hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Explain in detail the passive elements and active elements.
b) By using Thevenin's theorem shown in figure 1, find the current in 6Ω resistor. [8+7]

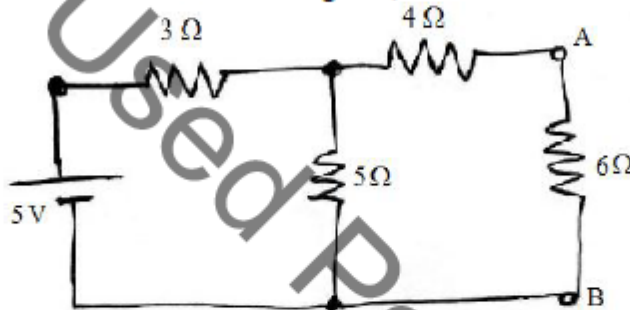


Figure 1

- 2.a) State Kirchhoff's voltage and current laws, Explain in detail.
b) By using superposition theorem, find the current flowing through 2Ω resistor. (Figure 2) [8+7]

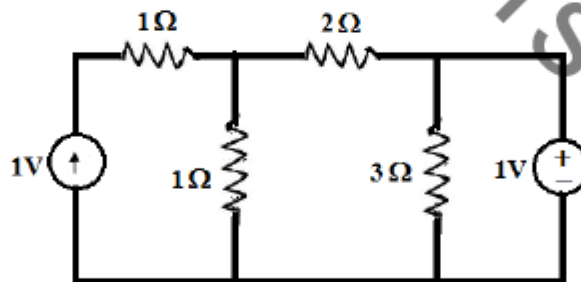


Figure 2

- 3.a) Explain the following terms of AC circuits
(i) rms value (ii) average value (iii) peak value
(iv) formfactor (v) phasor (vi) phase difference
b) Analyze the series RL circuit with a neat sketch and also draw the phasor diagram. [8+7]
- 4.a) Derive the relation between phase voltage and line voltage of a balanced three phase star connected system.
b) A circuit consisting of three branches, Z_2 is in parallel with Z_3 the combination is in series with Z_1 having the values $Z_1=5+j15$, $Z_2=2.5+j5$ and $Z_3=2-j8$ connected across single phase, 100 V, 50 Hz supply. Find i) I_1 , I_2 and I_3 ii) V_1 and V_2 . [8+7]

- 5.a) The emf per turn of a 1- ϕ , 2200/220 V, 50 Hz transformer is approximately 12V. Calculate
- The number of primary and secondary turns, and
 - The net cross-sectional area of core for a maximum flux density of 1.5 T?
- b) Explain the losses in a Transformer; also derive the maximum efficiency condition of a transformer. [8+7]
- 6.a) Explain the significance of torque-slip and characteristics of 3-phase induction motor.
- b) Why three phase induction motor not rotating at synchronous speed, explain. [8+7]
- 7.a) Explain the types of batteries and its important characteristics.
- b) Define earthing also explain the purpose of earthing. [7+8]
- 8.a) Explain the constructional details of synchronous generators.
- b) Why single phase induction motors are not self starting motors? Explain. [7+8]

--ooOoo--