

Code No: 113AU

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, February/March - 2016****ELECTRONIC DEVICES AND CIRCUITS****(Common to EEE, ECE, CSE, EIE, IT, MCT)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Write the applications of photo diode. [2]
- b) What is meant by depletion region? [3]
- c) Define ripple factor and PIV. [2]
- d) Explain the necessity of filter circuit after the rectifier circuit. [3]
- e) Why we call BJT as a current Controlled Device? [2]
- f) Which of the BJT configurations are suitable for impedance matching applications. Why? [3]
- g) Define operating point. [2]
- h) Explain thermal stability. [3]
- i) Compare FET and BJT. [2]
- j) Draw small signal model of JFET. [3]

PART-B**(50 Marks)**

- 2.a) Define tunneling phenomenon. Explain how tunnel diode operates under different operating conditions. In what way it is different from conventional diodes? Give the necessary energy level diagrams.
- b) Zener diode can be used as a voltage regulator. Justify it. [6+4]

OR

- 3.a) With the help of V-I characteristics, explain SCR operation.
- b) Derive the expression for Diffusion capacitance of a diode. [5+5]
- 4.a) A sinusoidal voltage whose $V_m=12V$ is applied to half-wave rectifier. The diode may be considered to be ideal and $R_L=1.5 K\Omega$ is connected as load. Find out peak value of current, RMS value of Current, DC value of current and Ripple factor.
- b) Derive the expression for Ripple factor for Full Wave Rectifier with L-Section filter. [6+4]

OR

5. Draw the circuit diagram and explain the operation of full wave rectifier using center tap transformer and using bridge rectifier without center tap transformer. Obtain the expression for peak inverse voltages of both. [10]

6.a) With neat diagram explain the construction, working characteristics of UJT. Give its equivalent circuit.

b) Explain about Punch through and Base width modulation. [5+5]

OR

7. Write a note on:

a) Transistor construction.

b) Voltage gain and current gain expression for CB configuration using transistor hybrid model. [4+6]

8.a) In a Silicon transistor circuit with a fixed bias, $V_{CC}=9V$, $R_C=3K\Omega$, $R_B=8K\Omega$, $\beta = 50$, $V_{BE}=0.7V$. Find the operating point and Stability factor.

b) What is the necessity of biasing circuits? Derive the expression for stability factor of self bias circuit. [5+5]

OR

9.a) The hybrid parameters for a transistor used in CE configuration are $h_{ie} = 5k\Omega$; $h_{fe} = 180$; $h_{re} = 1.25 \times 10^{-4}$; $h_{oe} = 16 \times 10^{-6}$ ohms. The transistor has a load resistance of $20 K\Omega$ in the collector and is supplied from a signal source of resistance $5 K\Omega$. Compute the value of input impedance, output impedance, current gain and voltage gain.

b) Give the advantages of h-parameter analysis. [7+3]

10.a) Write the construction, operation and characteristic behavior of JFET under various biasing conditions.

b) Draw and explain small-signal model of a MOSFET. [6+4]

OR

11.a) Describe the operation of common drain FET amplifier and derive the equation for voltage gain.

b) Explain the operation of Depletion mode MOSFET in detail. [5+5]

---ooOoo---

Code No: 113AU

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, November/December - 2017****ELECTRONIC DEVICES AND CIRCUITS****(Common to EEE, ECE, CSE, EIE, IT, MCT)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) For what voltage will the reverse current in p-n junction Germanium diode reach 90% of its saturation value at room temperature? [2]
- b) Write a short note on Varactor diode. [3]
- c) Derive the ripple factor for full wave rectifier. [2]
- d) Explain voltage regulation using zener diode. [3]
- e) Explain how transistor acts as an amplifier. [2]
- f) Give the Comparisons between CB, CE, CC configurations. [3]
- g) Define thermal runaway. [2]
- h) Compare all the three biasing circuits. [3]
- i) For a p-channel Silicon FET, with effective width 'a'= 2×10^{-4} cm and channel resistivity $\rho = 10 \Omega$. Find the pinch off voltage. [2]
- j) Draw the circuit diagram of fixed bias arrangement of a JFET. [3]

PART-B**(50 Marks)**

- 2.a) Explain PN diode characteristics in forward bias and reverse bias regions.
- b) Find the width of the depletion layer in a germanium junction diode which has the following specifications: Area $A = 0.001 \text{ cm}^2$, $\sigma_n = 1 \text{ mhos / cm}$, $\mu_n = 3800 \text{ cm}^2/\text{sec}$, $\mu_p = 1800 \text{ cm}^2/\text{sec}$. [5+5]

OR

- 3.a) Explain tunnel diode operation with the help of energy band diagrams.
- b) Explain the static characteristics of SCR. [5+5]
- 4.a) A full wave rectifier circuit with C-type capacitor filter is to supply a D.C. Current of 20 mA at 16V. If frequency is 50 Hz ripple allowed is 5%. Calculate:
 - i) Required secondary voltage of the transformer.
 - ii) Ratio of $I_{\text{peak}} / I_{\text{max}}$ through diodes and the value of C required.
- b) With a neat circuit diagram and necessary wave forms explain the operation of half wave rectifier. [5+5]

OR

- 5.a) An ac supply of 220V is applied to a half wave rectifier circuit through a transformer with a turns ratio of 10:1. Assume the ideal diode. Find:
 - i) dc output voltage
 - ii) PIV.
- b) Compare half wave, full wave and bridge rectifier circuits. [5+5]

- 6.a) Explain CE configuration with the help of input and output characteristics.
b) A transistor is operated at a forward current of $2\mu\text{A}$ and with the collector open circuited. Calculate the junction voltages V_C and V_E , the collector to emitter voltage V_{CE} assuming $I_{CO} = 2\mu\text{A}$, $I_{EO} = 1.6\mu\text{A}$ and $\alpha_N = 0.98$. [5+5]

OR

- 7.a) Draw and explain h-parameter model of BJT.
b) Qualitatively explain the static V-I characteristics of UJT. [5+5]
- 8.a) Explain the need for biasing in electronic circuits. What are the factors affecting the stability factor.
b) A transistor with $\beta = 100$ is to be used in Common Emitter Configuration with collector to base bias. The collector circuit resistance is $R_C = 1\text{k}\Omega$ and $V_{CC} = 10\text{V}$. Assume $V_{BE} = 0$.
i) Choose R_B so that the quiescent collector to emitter voltage is 4V .
ii) Find the stability factor. [5+5]

OR

- 9.a) Determine the quiescent currents and the collector to emitter voltage for a Ge transistor with $\beta = 50$ in the self biasing arrangements. The circuit component values are $V_{CC} = 20\text{V}$, $R_C = 2\text{k}\Omega$, $R_e = 0.1\text{k}\Omega$, $R_1 = 100\text{k}\Omega$ and $R_2 = 5\text{k}\Omega$. Find the stability factor S .
b) Explain the terms Bias Stabilization and Bias Compensation. [5+5]

- 10.a) Derive the expression for the width of depletion region 'W' in the case of p-channel JFET.
b) Explain the working of a depletion type MOSFET with a neat construction diagram and its characteristics. [5+5]

OR

11. Draw the circuit of source follower Amplifier and derive the expressions for A_I , A_V , R_i and R_o . [10]

---ooOoo---

Code No: 113AU

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech II Year I Semester Examinations, April/May - 2018****ELECTRONIC DEVICES AND CIRCUITS****(Common to EEE, ECE, CSE, EIE, IT, MCT)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Define static resistance. [2]
- b) Write the effect of temperature on diode characteristics. [3]
- c) What is regulation? [2]
- d) List the differences between different filters. [3]
- e) Define current amplification factor. [2]
- f) What is emitter follower? Draw the circuit diagram of CC configuration. [3]
- g) What is the need of biasing? [2]
- h) Explain, how to avoid thermal runaway? [3]
- i) Mention the applications of FET. [2]
- j) Why the input impedance of FET is higher than BJT? [3]

PART-B**(50 Marks)**

- 2.a) Draw and explain V-I characteristics of PN diode.
 - b) With suitable expressions explain transition capacitance. [5+5]
- OR**
- 3.a) Describe the principle of operation of tunnel diode.
 - b) Explain the working of semiconductor photo diode. [5+5]
- 4.a) Derive the equation for ripple factor of half wave rectifier with C-filter.
 - b) With suitable wave forms explain bridge rectifier. [5+5]
- OR**
- 5.a) Describe the operation of full wave rectifier with π -section filter.
 - b) A 50 Hz transformer having 60 V r. m. s. on each side of the centre tap supplies a full wave rectifier circuit. The circuit load is 210Ω with a shunt capacitor filter of $1000 \mu\text{F}$. Find the ripple factor. [5+5]
- 6.a) Explain the working of PNP transistor.
 - b) Write the differences between CB, CE, and CC Amplifier Configurations. [5+5]
- OR**
- 7.a) Derive the relation between α and β .
 - b) Discuss, how the h-parameters are determined from transistor Characteristics. [4+6]

- 8.a) Derive the equation for stability factor for fixed bias.
b) Draw and explain the circuit for bias compensation using diode. [5+5]

OR

- 9.a) Write a short note on Stabilization against variations in V_{BE} and β .
b) For the transistor amplifier circuit, when signal changes by 0.012 V, the base current changes by 9 μA and collector current by 1.3 mA. If the collector load $R_C = 6 \text{ K}\Omega$, $R_L = 12 \text{ K}\Omega$. Determine input resistance, current gain and voltage gain. [5+5]

- 10.a) Write short notes on Small Signal Model of JFET.
b) Draw and explain drain and transfer characteristics of depletion type MOSFET. [5+5]

OR

- 11.a) With neat sketch, discuss about common source FET amplifier.
b) Explain, how FET is working as Voltage Variable Resistor? [6+4]

---ooOoo---

Department Vision & Mission

Vision of the Department:

To evolve into a center of excellence in Electronics & Communications Engineering through creative and innovative practices in teaching-learning and Research in consonance with the contemporary and future needs of the country.

Mission of the Department:

To realize the department's vision, various academic and extra-curricular activities will be organized. The goal of these activities will be to:

- i.** To inspire and encourage development of key ideas and innovations that can contribute to socio-economic development of India as well as world.
- ii.** To identify and collaborate with experts, professionals, academicians, commercial and various governmental bodies and develop an environment conducive to research and development.
- iii.** To offer state-of-the-art programs that inspires and motivates students in perusing the role of researchers and developers through higher learning programs.



NRCM

your roots to success...

PROGRAMME EDUCATIONAL OBJECTIVES (PEOs)

PEOs:

PEO-I: (Core competence – Discipline knowledge) To motivate and mold students in to world class professionals by cultivating a fundamental desire to learn and apply the acquired skill sets in complex constrains being faced by our social infrastructure.

PEO-II :(Preparation – Employment/Higher studies) To encourage students in striving for higher cognitive aspirations where they will actively participate in quality improvement of academic and industrial components of our society.

PEO-III: (Professionalism – Professional value-knowledge development) To enlighten students and help them in understanding their role as professionals who are well groomed, ethically poised, mentally strong, passionate human beings and upstanding citizens.



your roots to success...

PROGRAM OUTCOMES (POs)


| | |
|----|--|
| 1 | Engineering knowledge: Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems |
| 2 | Problem analysis: Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences. |
| 3 | Design/development of solutions: Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations. |
| 4 | Conduct investigations of complex problems: Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions. |
| 5 | Modern tool usage: Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations. |
| 6 | The engineer and society: Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice. |
| 7 | Environment and sustainability: Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development. |
| 8 | Ethics: Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice. |
| 9 | Individual and team work: Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings. |
| 10 | Communication: Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions. |
| 11 | Project management and finance: Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments. |
| 12 | Life-long learning: Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change. |

PROGRAM SPECIFIC OUTCOMES (PSOs)

PSO1: Enabling the students to apply the knowledge of algorithm analysis, modeling, circuit design and verification methodologies to use and manage electro-mechanical systems that are integral part of modern socio-economic framework.

PSO2: Students will be able to examine the limitations of current implementation strategies and propose modifications and new ideas by using state-of-the-art tool chain in electronic communication systems.

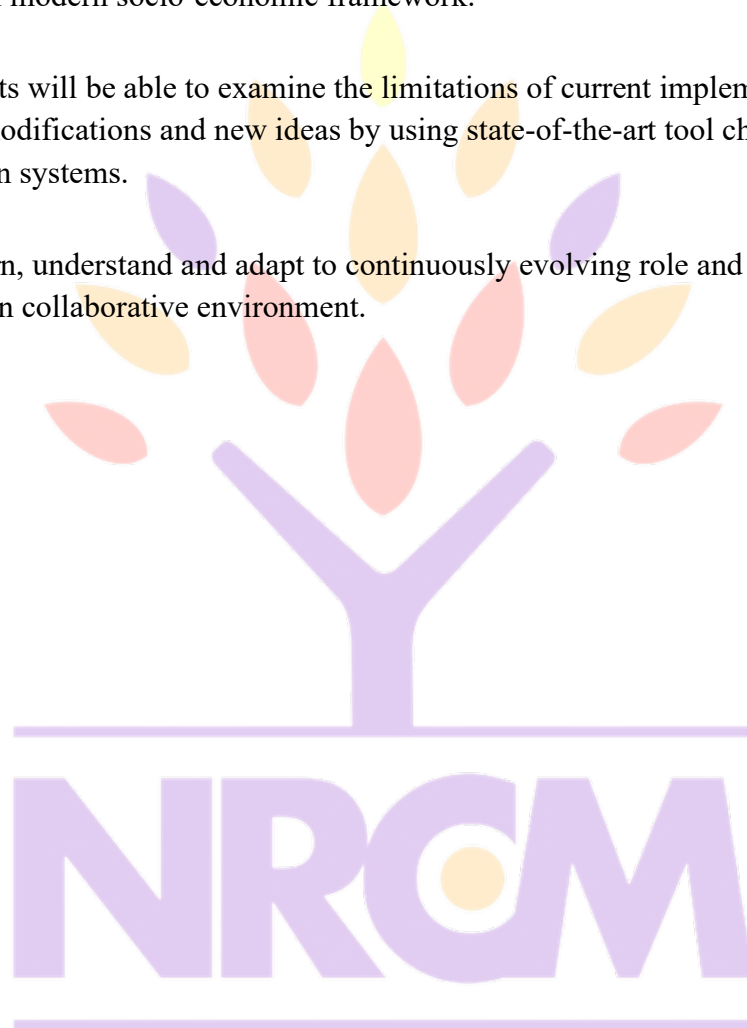PSO3: To learn, understand and adapt to continuously evolving role and ethical needs of professionals in collaborative environment.



your roots to success...

REVISED Bloom's Taxonomy Action Verbs

| Definitions | I. Remembering | II. Understanding | III. Applying | IV. Analyzing | V. Evaluating | VI. Creating |
|---------------------------|---|--|--|--|--|--|
| Bloom's Definition | Exhibit memory of previously learned material by recalling facts, terms, basic concepts, and answers. | Demonstrate understanding of facts and ideas by organizing, comparing, translating, interpreting, giving descriptions, and stating main ideas. | Solve problems to new situations by applying acquired knowledge, facts, techniques and rules in a different way. | Examine and break information into parts by identifying motives or causes. Make inferences and find evidence to support generalizations. | Present and defend opinions by making judgments about information, validity of ideas, or quality of work based on a set of criteria. | Compile information together in a different way by combining elements in a new pattern or proposing alternative solutions. |



your roots to success...



NARSIMHA REDDY ENGINEERING COLLEGE

UGC AUTONOMOUS INSTITUTION

Maisammaguda (V), Kompally - 500100, Secunderabad, Telangana State, India

UGC - Autonomous Institute
Accredited by NBA & NAAC with 'A' Grade
Approved by AICTE
Permanently affiliated to JNTUH



ACADEMIC CALENDAR :: 2023-24 B.TECH I YEAR I & II SEMESTER

I SEM


| S.No. | Description | Duration | | Duration (Weeks) |
|-------|---|------------|------------|------------------|
| | | From | To | |
| 1 | Commencement of I Semester class work | 26.08.2023 | | |
| 2 | Induction Program | 26.08.2023 | 05.09.2023 | 2 |
| 3 | 1 st Spell of Instructions (Including Dussehra Recess) | 07.09.2023 | 08.11.2023 | 9 |
| 4 | First Mid Term Examinations | 09.11.2023 | 15.11.2023 | 1 |
| 5 | 2 nd Spell of Instructions | 16.11.2023 | 17.01.2024 | 9 |
| 6 | Second Mid Term Examinations | 18.01.2024 | 24.01.2024 | 1 |
| 7 | End Semester Examinations | 25.01.2024 | 07.02.2024 | 2 |
| 8 | Lab Examinations | 08.02.2024 | 14.02.2024 | 1 |

II SEM

| S.No. | Description | Duration | | Duration (Weeks) |
|-------|---|------------|------------|------------------|
| | | From | To | |
| 1 | Commencement of II Semester class work | 19.02.2024 | | |
| 2 | 1 st Spell of Instructions | 19.02.2024 | 13.04.2024 | 8 |
| 3 | First Mid Term Examinations | 15.04.2024 | 20.04.2024 | 1 |
| 4 | 2 nd Spell of Instructions (Including Summer Vacation) | 22.04.2024 | 29.06.2024 | 10 |
| 5 | Second Mid Term Examinations | 01.07.2024 | 06.07.2024 | 1 |
| 6 | End Semester Examinations | 08.07.2024 | 20.07.2024 | 2 |
| 7 | Lab Examinations | 22.07.2024 | 27.07.2024 | 1 |

Copy to:

1. Deans
2. IQAC
3. All HODs
4. Administrative Officer
5. Account officer
6. Web Portal I/C
7. ERP I/C
8. Library
9. Student Notice Boards


PRINCIPAL
NARSIMHA REDDY ENGINEERING COLLEGE
UGC AUTONOMOUS
Survey No.518, Maisammaguda (V), Dhulapaliy (P),
Medchal (M), Medchal Dist., Hyderabad-500100

SYLLABUS

ELECTRONIC DEVICES AND CIRCUITS

B.Tech. I Year I Sem.

L T P C

2 0 0 2

Course Objectives:

1. To introduce components such as diodes, BJTs and FETs.
2. To know the applications of devices.
3. To know the switching characteristics of devices.

Course Outcomes: Upon completion of the Course, the students will be able to:

1. Acquire the knowledge of various electronic devices and their use on real life.
2. Know the applications of various devices.
3. Acquire the knowledge about the role of special purpose devices and their applications.

| Course | PO1 | PO2 | PO3 | PO4 | PO5 | PO6 | PO7 | PO8 | PO9 | PO10 | PO11 | PO12 |
|--------|-----|-----|-----|-----|-----|-----|-----|-----|-----|------|------|------|
| CO1 | 3 | 1 | 2 | - | - | 1 | 1 | - | - | - | - | 1 |
| CO2 | 3 | 2 | 3 | - | - | 2 | 1 | - | - | - | - | 1 |
| CO3 | 3 | 3 | 3 | - | - | 2 | 1 | - | - | - | - | 1 |

UNIT - I

Diodes: Diode - Static and Dynamic resistances, Equivalent circuit, Diffusion and Transition Capacitances, V-I Characteristics, Diode as a switch- switching times.

UNIT - II

Diode Applications: Rectifier - Half Wave Rectifier, Full Wave Rectifier, Bridge Rectifier, Rectifiers with Capacitive and Inductive Filters, Clippers-Clipping at two independent levels, Clamper-Clamping Circuit Theorem, Clamping Operation, Types of Clampers.

UNIT - III

Bipolar Junction Transistor (BJT): Principle of Operation, Common Emitter, Common Base and Common Collector Configurations, Transistor as a switch, switching times,

UNIT - IV

Junction Field Effect Transistor (FET): Construction, Principle of Operation, Pinch-Off Voltage, Volt- Ampere Characteristic, Comparison of BJT and FET, FET as Voltage Variable Resistor, MOSFET, MOSTET as a capacitor.

UNIT - V

Special Purpose Devices: Zener Diode - Characteristics, Zener diode as Voltage Regulator, Principle of Operation - SCR, Tunnel diode, UJT, Varactor Diode, Photo diode, Solar cell, LED, Schottky diode.

TEXT BOOKS:

1. Jacob Millman - Electronic Devices and Circuits, McGraw Hill Education
2. Robert L. Boylestead, Louis Nashelsky- Electronic Devices and Circuits theory, 11th Edition, 2009, Pearson.

REFERENCE BOOKS:

1. Horowitz -Electronic Devices and Circuits, David A. Bell – 5th Edition, Oxford.
2. Chinmoy Saha, Arindam Halder, Debaati Ganguly - Basic Electronics-Principles and Applications, Cambridge, 2018



your roots to success...

MAPPING OF COURSE OUTCOMES (CO) WITH PO'S & PSO'S MATRIX:

| Course Outcome s (CO's) | Program Outcomes (PO's) | | | | | | | | | | | |
|----------------------------------|----------------------------|---------|-----|---------|---------|---------|---------|-----|---------|----------|----------|------|
| | PO 1 | PO 2 | PO3 | PO 4 | PO 5 | PO 6 | PO 7 | PO8 | PO 9 | PO1 0 | PO1 1 | PO12 |
| CO1 | 3 | 1 | 2 | - | 1 | 1 | - | - | - | - | - | 1 |
| CO2 | 3 | 2 | 3 | - | 2 | 1 | - | - | - | - | - | 1 |
| CO3 | 3 | 2 | 3 | - | 2 | 1 | - | - | - | - | - | 1 |
| CO4 | 2 | 2 | 3 | - | 2 | 1 | - | - | - | - | - | 1 |
| CO5 | 2 | 2 | 3 | - | 2 | 1 | - | - | - | - | - | 1 |

| Course Outco mes (CO's) | Program Specific Outcomes (PSO's) | | |
|----------------------------------|-----------------------------------|------|------|
| | PSO1 | PSO2 | PSO3 |
| CO1 | 3 | 2 | |
| CO2 | 2 | 2 | |
| CO3 | 3 | 2 | |
| CO4 | 2 | 2 | |
| CO5 | 2 | 2 | |

your roots to success...



NOMINAL SHEET

IECE-A

| S.NO | ROLL NO | NAME OF THE STUDENT |
|------|------------|------------------------------|
| 1 | 23X01A0401 | AADHIMULLA SAI RITHUN |
| 2 | 23X01A0402 | ABBAGONI SATHVIKA |
| 3 | 23X01A0403 | AKULA SAI KOUSHIK |
| 4 | 23X01A0404 | ALETI SIRISHA |
| 5 | 23X01A0405 | ANAGANDULA SHIVAKUMAR |
| 6 | 23X01A0406 | ANNAPUREDDY MANIKANTA REDDY |
| 7 | 23X01A0407 | ANTHIREDDY GARI SRIPAL REDDY |
| 8 | 23X01A0408 | ANTHIREDDY GARI SRUTHI |
| 9 | 23X01A0409 | ANURAGAM KARTHIKEYA |
| 10 | 23X01A0410 | B PURUSHOTHAM |
| 11 | 23X01A0411 | BABU SANDEEP |
| 12 | 23X01A0412 | BALUSA THANISH KUMAR |
| 13 | 23X01A0413 | BANDA MANIKANTA |
| 14 | 23X01A0414 | BATTHULA SRIDHAR |
| 15 | 23X01A0415 | BETHI SATHWIKA |
| 16 | 23X01A0416 | BHEEMA HARI CHARAN |
| 17 | 23X01A0417 | BHIMIREDDY RADHA |
| 18 | 23X01A0418 | BHUSA VAISHNAVI |
| 19 | 23X01A0419 | BODAKUNTA SOWMIKA |
| 20 | 23X01A0420 | BODANAMU SREEDHAR |
| 21 | 23X01A0421 | bontha anuk |
| 22 | 23X01A0422 | BOORLA AMULYA |
| 23 | 23X01A0423 | BOORUGUPALLY NEELIMA |
| 24 | 23X01A0424 | BUDDE ROHINI |
| 25 | 23X01A0425 | BUKA VINAY |
| 26 | 23X01A0426 | BUNNE PREETHAM DATTA |
| 27 | 23X01A0427 | CHAUDHARI SOHAM |
| 28 | 23X01A0428 | CHEDADEEPU PAVAN |
| 29 | 23X01A0429 | CHELLAM VIKAS |
| 30 | 23X01A0430 | CHILUKA SRIHARI |
| 31 | 23X01A0431 | CHINDE DILEEP KUMAR |
| 32 | 23X01A0432 | CHINTHALA UDHAYA SRI |
| 33 | 23X01A0433 | DOMADI ARAVIND |
| 34 | 23X01A0434 | DULAM AKSHARA |
| 35 | 23X01A0435 | DUNDIGELA LIKHITHA |
| 36 | 23X01A0436 | EMBARI LOHITH |
| 37 | 23X01A0437 | ETTABOINA HARI KRISHNA |
| 38 | 23X01A0438 | GADARI KALYANI |
| 39 | 23X01A0439 | GADDAM HARSHITH REDDY |

| S.NO | ROLL NO | NAME OF THE STUDENT |
|------|------------|---------------------------|
| 40 | 23X01A0440 | GADDAM SRIVARSHA |
| 41 | 23X01A0441 | GADDAM SURASHMIKA |
| 42 | 23X01A0442 | GAITHINI BHANUPRASAD |
| 43 | 23X01A0443 | GOLAKOTI VIKAS |
| 44 | 23X01A0444 | GOLLA AKHIL |
| 45 | 23X01A0445 | GOLLA SHIVAKUMAR |
| 46 | 23X01A0446 | GOLLAPALLI GOPI KRISHNA |
| 47 | 23X01A0447 | GUDURI SAI PRASAD |
| 48 | 23X01A0448 | GUDURU LAKSHMI PATHI |
| 49 | 23X01A0449 | K J LASYA |
| 50 | 23X01A0450 | KADARI BHARATH |
| 51 | 23X01A0451 | KADARI SAGAR |
| 52 | 23X01A0452 | KADUDULA NANDA KISHORE |
| 53 | 23X01A0453 | KANJARLA VAISHNAVI |
| 54 | 23X01A0454 | KATHI SATHYA SAI SRAVANTH |
| 55 | 23X01A0455 | KATPALLY DINESH REDDY |
| 56 | 23X01A0456 | KEESARI MAHESH KUMAR |
| 57 | 23X01A0457 | KODIGELA MADHURI |
| 58 | 23X01A0458 | KOLA GOWTHAM |
| 59 | 23X01A0459 | KOLI SRIJA |
| 60 | 23X01A0460 | KONAPOLU RAJESH |
| 61 | 23X01A0461 | KONDA NITHYASRI |
| 62 | 23X01A0462 | KOTA CHANDU |
| 63 | 23X01A0463 | KOTHAPALLY MAHENDHAR |
| 64 | 23X01A0464 | KOTHAPALLY NIKHIL |

NOMINAL SHEET

IECE-B

| S.NO | ROLL NO | NAME OF THE STUDENT |
|------|------------|---------------------------------|
| 1 | 23X01A0465 | KOTTALA KARTHIK |
| 2 | 23X01A0466 | KUNAPARAJU LAKSHMI SAI SOWJANYA |
| 3 | 23X01A0467 | KUNDENA SAI PRASAD |
| 4 | 23X01A0468 | KYATHAM RUSHIKESH |
| 5 | 23X01A0469 | LINGALA SAI CHARAN |
| 6 | 23X01A0470 | M KEERTHANA |
| 7 | 23X01A0471 | MALICHALIMA SHASHANK |
| 8 | 23X01A0472 | MALLARAM SAI TEJA |
| 9 | 23X01A0473 | MALLARAM SRIRAM REDDY |
| 10 | 23X01A0474 | MALLEPOOLA HEMANTH GOUD |
| 11 | 23X01A0475 | MANNAPURAM SPANDANA |
| 12 | 23X01A0476 | METHRY DHANUSH |
| 13 | 23X01A0477 | MIRUPALA MANOJ |
| 14 | 23X01A0478 | MITTAPALLI SHASHANK |
| 15 | 23X01A0479 | MYSANOLLA SRAVANTHI |
| 16 | 23X01A0480 | NAIDI PAVAN |
| 17 | 23X01A0481 | NAKKIRTHI GOUTHAM |
| 18 | 23X01A0482 | NALLANAGULA HARSHINI |
| 19 | 23X01A0483 | NAYAKA JAGADHISH |
| 20 | 23X01A0484 | NUKALA SREEVALLI SARVANI |
| 21 | 23X01A0485 | PALAMAKULA AKHILA |
| 22 | 23X01A0486 | PEDDAKONDRILLA POOJITHA REDDY |
| 23 | 23X01A0487 | PEDDOLLA RISHANK REDDY |
| 24 | 23X01A0488 | PERAM VENKATESWARLU |
| 25 | 23X01A0489 | PERUKA MAHESH |
| 26 | 23X01A0490 | PERUKA THANUSHA |
| 27 | 23X01A0491 | PILLI VARUN |
| 28 | 23X01A0492 | POLAKI PAVANI |
| 29 | 23X01A0493 | PORLA VAMSHI KUMAR |
| 30 | 23X01A0494 | RAO GREESHMA |
| 31 | 23X01A0495 | RAVIKANTI AKSHITHA |
| 32 | 23X01A0496 | RAVULAPALLI RAMA KRISHNA REDDY |
| 33 | 23X01A0497 | SAMBARI VENKAT SAI |
| 34 | 23X01A0498 | SAMOD RUTHUJA |
| 35 | 23X01A0499 | SANGI SUMUKH |
| 36 | 23X01A04A0 | SESHAM PRATHIBHA |
| 37 | 23X01A04A1 | SHAIK MD SHABBIER |
| 38 | 23X01A04A2 | SIRIPURAM SRIJA |
| 39 | 23X01A04A3 | SRIRAMA SRITHI |



NARSIMHA REDDY ENGINEERING COLLEGE

UGC AUTONOMOUS INSTITUTION

Maisammaguda (V), Kompally - 500100, Secunderabad, Telangana State, India

UGC - Autonomous Institute
Accredited by NBA & NAAC with 'A' Grade
Approved by AICTE
Permanently affiliated to JNTUH

| S.NO | ROLL NO | NAME OF THE STUDENT |
|------|------------|--------------------------------|
| 40 | 23X01A04A4 | SURGU VISHAL GOUD |
| 41 | 23X01A04A5 | TAMMALI MUKESH |
| 42 | 23X01A04A6 | TAMMEVAR SACHIN |
| 43 | 23X01A04A7 | TAMMISETTI HARSHITH |
| 44 | 23X01A04A8 | THAVITI MANIDEEP |
| 45 | 23X01A04A9 | THOTTE NITHIN |
| 46 | 23X01A04B0 | TIPPY REDDY PRANAVI |
| 47 | 23X01A04B1 | TOKALA VENKATA SIVA NAGA RAJU |
| 48 | 23X01A04B2 | TUNGENA NAVYA |
| 49 | 23X01A04B3 | UDI HARISH |
| 50 | 23X01A04B4 | UPPUGALLA THARUN KUMAR |
| 51 | 23X01A04B5 | URA RATHAN KUMAR |
| 52 | 23X01A04B6 | VANGA VAIBHAV REDDY |
| 53 | 23X01A04B7 | VANGALA MEGHA SHYAM REDDY |
| 54 | 23X01A04B8 | VELPUR NAVATEJ |
| 55 | 23X01A04B9 | VEMULA REVANTH |
| 56 | 23X01A04C0 | VEMULA SAI KARTHIK |
| 57 | 23X01A04C1 | VETUKURI SAIVARMA |
| 58 | 23X01A04C2 | VUPPUNUTULA HARSHAVARDHAN GOUD |
| 59 | 23X01A04C3 | VUTAKURI VASUNDHARA |
| 60 | 23X01A04C4 | VUTNOOR MANIDHAR |
| 61 | 23X01A04C5 | YARAVEDA VENKATREDDY |
| 62 | 23X01A04C6 | YEDDI NITHYA SRI |
| 63 | 23X01A04C7 | YELETI SHREYAN REDDY |
| 64 | 23X01A04C8 | YERAVEDA JANARDHAN REDDY |

NRCM

your roots to success...

NOMINAL SHEET

I CSC A

| S.NO | ROLL NO | NAME OF THE STUDENT |
|------|------------|-----------------------------|
| 1 | 23X01A6201 | AAKULA VARUN MALLIK GOUD |
| 2 | 23X01A6202 | AAREPALLY GEETHA |
| 3 | 23X01A6203 | ADAPA DURGA SATYA SAI PAVAN |
| 4 | 23X01A6204 | AKKIREDDY SHIREESHA |
| 5 | 23X01A6205 | ALLANKI SIDDHARTHA GOUD |
| 6 | 23X01A6206 | AMBATI POOJITHA |
| 7 | 23X01A6207 | AMKOLE BHARATH KUMAR |
| 8 | 23X01A6208 | ANDHE MANIL REDDY |
| 9 | 23X01A6209 | ANKAPURAM VINDHYA REDDY |
| 10 | 23X01A6210 | ANUMANDLA ANVESH |
| 11 | 23X01A6211 | AREMPULA MAHESH |
| 12 | 23X01A6212 | ARKALA MOUNIKA |
| 13 | 23X01A6213 | ARRELI BHARATH |
| 14 | 23X01A6214 | BADDAM SWETHA REDDY |
| 15 | 23X01A6215 | BADEPALLY SRUJANA |
| 16 | 23X01A6216 | BADISHA SANDHYA |
| 17 | 23X01A6217 | BANOTHU PREM KUMAR |
| 18 | 23X01A6218 | BATTU MANIDEEP |
| 19 | 23X01A6219 | BATTUPALLI CHARAN |
| 20 | 23X01A6220 | BAWAJI YASWANTH KUMAR |
| 21 | 23X01A6221 | BAYAGANI MANIDEEP |
| 22 | 23X01A6222 | BHANUVARUN GONTYALA |
| 23 | 23X01A6223 | BHUTHAPALLY BALAJI |
| 24 | 23X01A6224 | BIRUDURAJU ASHWITHRAJU |
| 25 | 23X01A6225 | BOGGULA RAJU |
| 26 | 23X01A6226 | BOLLU REVANTH |
| 27 | 23X01A6227 | BOOSA PRAVEEN |
| 28 | 23X01A6228 | BOPPA NISHANTH |
| 29 | 23X01A6229 | BUDDE DINESH |
| 30 | 23X01A6230 | BUNNI SHIVA PRASAD |
| 31 | 23X01A6231 | BURRA ASHWITH |
| 32 | 23X01A6232 | BURRA SHIVADIKSHITHA |
| 33 | 23X01A6233 | BUSI NAGESH |
| 34 | 23X01A6234 | CH SHIVA PRASAD |
| 35 | 23X01A6235 | CHADA YESHWANTH |



NARSIMHA REDDY ENGINEERING COLLEGE

UGC AUTONOMOUS INSTITUTION

Maisammaguda (V), Kompally - 500100, Secunderabad, Telangana State, India

UGC - Autonomous Institute
Accredited by NBA & NAAC with 'A' Grade
Approved by AICTE
Permanently affiliated to JNTUH

| S.NO | ROLL NO | NAME OF THE STUDENT |
|------|------------|---------------------------|
| 36 | 23X01A6236 | CHALLA GEETHIKA |
| 37 | 23X01A6237 | CHEKKILLA SHIVANI |
| 38 | 23X01A6238 | CHELIMALA HARISH REDDY |
| 39 | 23X01A6239 | CHINTHAKINDI MANASA |
| 40 | 23X01A6240 | CHINTHAKULA REVATHI |
| 41 | 23X01A6241 | CHOWDOJU MANASWI |
| 42 | 23X01A6242 | DADIGALA PRAVEEN |
| 43 | 23X01A6243 | DAMMANNAGARI SHIVASREE |
| 44 | 23X01A6244 | DEBBATI MANOHAR |
| 45 | 23X01A6245 | DODDANNAGARI VAMSHI REDDY |
| 46 | 23X01A6246 | DOGGALA ANUSH |
| 47 | 23X01A6247 | DONGA JAYA SATYA KARTHIK |
| 48 | 23X01A6248 | DONTHI HARSHITHA |
| 49 | 23X01A6249 | DORNALA VIGNESH |
| 50 | 23X01A6250 | DUNDIGAL VISHALI |
| 51 | 23X01A6251 | DUPETI SAI KUMAR |
| 52 | 23X01A6252 | DURGAM USHASRI |
| 53 | 23X01A6253 | DYAVANAPELLY PRADEEP |
| 54 | 23X01A6254 | ELIGETI SHIVA KUMAR |
| 55 | 23X01A6255 | ELKUSI RAJKUMAR |
| 56 | 23X01A6256 | ELLENDULA DHIRAJ |
| 57 | 23X01A6257 | ERAM DEEPIKA |
| 58 | 23X01A6258 | GADDAM RUTHIKA REDDY |
| 59 | 23X01A6259 | GADDAM SRIHITHA |
| 60 | 23X01A6260 | GANNOJU SUSHMITHA |
| 61 | 23X01A6261 | GODI SPURTHI |
| 62 | 23X01A6262 | GOPATHI ROHAN |
| 63 | 23X01A6263 | GUNDALA JAGADEESHWAR |
| 64 | 23X01A6264 | HARSHAVARDHAN VELISHOJU |
| 65 | 23X01A6265 | ILAPURAM RAJASHEKAR |

your roots to success...

TIME TABLE

| EDC | | | | | | | |
|------------|------------|-------------|-------------|------------------------|-----------|-----------|-----------|
| | 9:30-10:30 | 10:30-11:30 | 11:30-12:20 | 12:20-1:10 | 1.10-2.10 | 2.10-3.10 | 3.10-4.00 |
| | 1 | 2 | 3 | | 4 | 5 | 6 |
| Mon | | ECE B | | Lunch break | | | |
| Tue | | CSC A | | | | | |
| Wed | | ECE B | ECE A | | | | CSC A |
| Thu | | | | | | | ECE A |
| Fri | | | | | | | |
| Sat | ECE A | | CSC A | | | ECE B | |



your roots to success...

LESSON PLAN

UNIT-I

Learning Objectives:

- To understand the definitions static and dynamic resistances
- To illustrate the Load line analysis
- To define Diffusion and transition capacitance and its derivation
- Explain how a diode acts a switch and its applications.

| S.No. | Description of Topic | No. of Hrs. required | Method of Teaching |
|-------------|---|----------------------|--------------------|
| 1. | Diode - Static and Dynamic resistances, | 2 | Black board |
| 2. | Equivalent circuit, Load line Analysis | 2 | Black board + PPT |
| 3. | Diffusion and Transition Capacitances | 2 | Black board + PPT |
| 4. | Diode Applications: Switch-Switching times. | 2 | Black board + PPT |
| 5 | Problems related to discussed topic | 2 | Black board |
| Total Hours | | 10 | |

your roots to success...

UNIT – II

Learning Objectives:

- To construct Rectifier and discuss their properties
- To construct Rectifiers with filters and discuss about them.
- To define Clipping and clamping and discuss their analysis

| S.No. | Description of Topic | No. of Hrs. required | Method of Teaching |
|-------|---|----------------------|--------------------|
| 1. | Rectifier - Half Wave Rectifier, Full Wave Rectifier, | 1 | Black board + PPT |
| 2. | Bridge Rectifier, | 2 | Black board + PPT |
| 3. | Rectifiers with Capacitive and Inductive Filters, | 1 | Black board + PPT |
| 4. | Clippers-Clipping at two independent levels, | 2 | Black board + PPT |
| 5. | Clamper-Clamping Circuit Theorem, | 1 | Black board + PPT |
| 6. | Clamping Operation, Types of Clampers. | 1 | Black board + PPT |
| 7. | Problems on rectifiers | 2 | Black board |
| | Total hours | 10 | |

UNIT-III

Learning Objectives:

- To Define BJT and its operation
- To discuss Transistor configurations and h- parameters
- To Construct transistor as a switch and discuss its switching times

| S.No. | Description of Topic | No. of Hrs. required | Method of Teaching |
|-------------|--|----------------------|--------------------|
| 1. | Principle of operation bjt | 2 | Black board + ppt |
| 2. | Common emitter configuration | 1 | Black board |
| 3. | Common base configuration | 1 | Black board + ppt |
| S.No. | Description of Topic | No. of Hrs. required | Method of Teaching |
| 4. | Common collector configuration | 1 | Black board + PPT |
| 5. | Difference between configurations | 1 | Black board + PPT |
| 6. | Transistor as a switch and switching timings | 1 | Black board + PPT |
| 7. | Problems related to BJT | 2 | Black board + PPT |
| Total Hours | | 09 | |

your roots to success...

UNIT-IV

Learning Objectives:

- To define JFET and its characteristics
- To construct and operation of FET
- Comparison of BJT and FET
- MOSFET AND ITS CONSTRUCTION

| S.No. | Description of Topic | No. of Hrs. required | Method of Teaching |
|-------------|--|----------------------|--------------------|
| 1. | Construction of JFET and its operation | 2 | Black board |
| 2. | Pinch off voltage, V-I characteristics | 2 | Black board |
| 3. | Comparison of BJT and FET | 1 | Black board |
| 4. | FET as voltage variable resistor | 1 | Black board |
| 5. | MOSFET introduction | 1 | Black board |
| 6. | MOSFET as a capacitor | 1 | Black board |
| 7. | Problems related to FET | 1 | Black board |
| Total Hours | | 09 | |

NRCM

your roots to success...

UNIT-V

Learning Objectives:

- To learn about special purpose devices and its characteristics
- Principle and its operation of zener diode, scr, varactor diode, photo diode.

| S.No. | Description of Topic | No. of Hrs. required | Method of Teaching |
|-------------|---|----------------------|--------------------|
| 1. | Zener diode- characteristics and zener as voltage regulator | 1 | Black board + PPT |
| 2. | Principle & operation -scr | 2 | Black board + PPT |
| 3. | Tunnel diode, UJT | 2 | Black board + PPT |
| 4. | Varactor diode, photo diode | 2 | Black board + PPT |
| 5. | Solar cell, led, schottky diode | 2 | Black board + PPT |
| Total hours | | 9 | |

Total Hours required

| UNIT | No. of Hours Required |
|---------------|-----------------------|
| UNIT-I | 10 |
| UNIT:2 | 10 |
| UNIT:3 | 09 |
| UNIT:4 | 09 |
| UNIT:5 | 9 |
| Total | 47 |

your roots to success...

QUESTION BANK
UNIT-I

| S.No | Questions | BT | CO | PO |
|--|--|----|----|----|
| Part – A (Short Answer Questions) | | | | |
| 1 | Define Static and Dynamic resistance of PN diode | 2 | 1 | 2 |
| 2 | What is meant by depletion region | 2 | 1 | 1 |
| 3 | For what voltage will the reverse current in pn ge diode reach 90%of its saturation value at room temperature | 2 | 1 | 1 |
| 4 | Write the effect of temperature on diode characteristics | 4 | 1 | 2 |
| 5 | Define static resistance | 3 | 1 | 2 |
| 8 | Draw the Diode Equivalent Circuit. Mention the applications of PN-junction diode. | 3 | 1 | 1 |
| 9 | Explain how P-N junction diode acts as a Rectifier. | 4 | 1 | 1 |
| Part – B (Long Answer Questions) | | | | |
| 10 | a) write short notes on load line analysis of PN Diode | 4 | 1 | 2 |
| | b) Explain the avalanche and Zener break down in PN diode | 3 | 1 | 3 |
| 11 | a) Derive the expression for Transition capacitance of PN Diode | 3 | 1 | 2 |
| | b) Derive the expression for diffusion capacitance of a diode | 3 | 1 | 1 |
| 12 | a) Explain PN diode characteristics in forward and reverse bias regions | 4 | 1 | 3 |
| | b) Find the width of the depletion layer in a germanium junction diode which has the following specifications: Area $A = 0.001 \text{ cm}^2$, $\sigma_n = 1 \text{ mhos / cm}$, $\mu_n = 3800 \text{ cm}^2/\text{sec}$, $\mu_p = 1800 \text{ cm}^2/\text{sec}$. [5+5] | 3 | 1 | 2 |
| 13 | a) Discuss switching characteristics of PN junction diode | 3 | 1 | 3 |

NRCM

your roots to success...

UNIT-II

| S.No | Questions | BT | CO | PO |
|--|---|----|----|----|
| Part – A (Short Answer Questions) | | | | |
| 1 | what is a rectifier and its types | 2 | 2 | 1 |
| 2 | Distinguish between series and shunt clippers | 2 | 2 | 1 |
| 3 | What is the necessity of filter. List the types of filters | 2 | 2 | 1 |
| 4 | Define regulation and efficiency of a rectifier. | 2 | 2 | 1 |
| 5 | Define ripple factor and PIV | 2 | 2 | 1 |
| 6 | Explain the necessity of filter circuit after the rectifier circuit | 2 | 2 | 1 |
| 7 | Derive the ripple factor for a full wave rectifier | 1 | 2 | 1 |
| 8 | List the difference between different filters | 1 | 2 | 1 |
| 9 | Define clampers | 2 | 2 | 1 |
| Part – B (Long Answer Questions) | | | | |
| 10 | a) A sinusoidal voltage whose $V_m=12V$ is applied to half-wave rectifier. The diode may be considered to be ideal and $R_L=1.5 K\Omega$ is connected as load. Find out peak value of current, RMS value of Current, DC value of current and Ripple factor. | 3 | 2 | 1 |
| | b) Derive the expression for Ripple factor for Full Wave Rectifier with L-Section filter. [6+4] | 3 | 2 | 2 |
| OR | | | | |
| 11 | a) Draw the circuit diagram and explain the operation of full wave rectifier using center tap transformer and using bridge rectifier without center tap transformer. Obtain the expression for peak inverse voltages of both. [10] | 4 | 2 | 3 |
| | b) A full wave rectifier circuit with C-type capacitor filter is to supply a D.C. Current of 20 mA at 16V. If frequency is 50 Hz ripple allowed is 5%. Calculate: i) Required secondary voltage of the transformer. ii) Ratio of I_{peak}/I_{max} through diodes and the value of C required. | 2 | 2 | 2 |
| 14 | a) With a neat circuit diagram and necessary wave forms explain the operation of half wave rectifier. [5+5] | 4 | 2 | 3 |
| | b) An ac supply of 220V is applied to a half wave rectifier circuit through a transformer with a turns ratio of 10:1. Assume the ideal diode. Find: i) dc output voltage ii) PIV. | 3 | 2 | 3 |
| 15 | a) Compare half wave, full wave and bridge rectifier circuits. | 2 | 2 | 2 |
| | b) Derive the expression for halfwave rectifier with c- filter | 2 | 2 | 2 |
| 16 | With suitable wave forms explain bridge rectifier | 2 | 2 | 2 |
| 17 | A 50 Hz transformer having 60 V r. m. s. on each side of the centre tap supplies a full wave rectifier circuit. The circuit load is 210 Ω with a shunt capacitor filter of 1000 μF . Find the ripple factor. [5+5] | 2 | 2 | 2 |

UNIT-III

| S.No | Questions | BT | CO | PO |
|--|---|----|----|----|
| Part – A (Short Answer Questions) | | | | |
| 1 | What is meant by thermal runaway? Explain. | 2 | 3 | 1 |
| 2 | What do you mean by early effect | 1 | 3 | 1 |
| 3 | Explain about collector feedback bias. | 2 | 3 | 1 |
| 4 | Compare CE, CB and CC configurations | 2 | 3 | 1 |
| 5 | What is the need of biasing? | 2 | 3 | 1 |
| 6 | Explain Bias Compensation using Diodes. | 2 | 3 | 1 |
| 7 | Explain the working of a transistor as a switch | 4 | 3 | 2 |
| 8 | Define alpha and beta DC amplification factors of BJT. | 2 | 3 | 2 |
| Part – B (Long Answer Questions) | | | | |
| 9 | With neat diagram explain various current components in an PNP bipolar junction transistor. | 3 | 3 | 1 |
| 10 | Draw and explain input and output characteristics of CB configuration | 2 | 3 | 1 |
| 11 | a) Draw and explain input and output characteristics of CE configuration | 4 | 3 | 2 |
| | b) Explain the different operating regions of transistor. | 2 | 3 | 3 |
| 12 | a) Draw and explain input and output characteristics of CC configuration | 3 | 3 | 3 |
| | b) Derive general equation for collector current I_c | 2 | 3 | 2 |

NRCM

your roots to success...

UNIT-IV

| S.No | Questions | BT | CO | PO |
|--|--|----|----|----|
| Part – A (Short Answer Questions) | | | | |
| 1 | Compare BJT and FET. | 2 | 4 | 1 |
| 2 | Explain classification of FET | 1 | 4 | 1 |
| 3 | Define Transconductance of FET | 2 | 4 | 1 |
| 4 | Define MOSFET how it is different from JFET | 2 | 4 | 1 |
| 5 | What is meant of enhancement MOSFET | 2 | 4 | 1 |
| 6 | What is meant of Depletion MOSFET | 2 | 4 | 1 |
| 7 | What is the input impedance of common source amplifier | 2 | 4 | 1 |
| 8 | For a p-channel Silicon FET, with effective width 'a'=2×10 ⁻⁴ cm and channel resistivity ρ =10 Ω. Find the pinch off voltage. | 1 | 4 | 2 |
| 9 | Explain how to avoid thermal runaway | 2 | 4 | 1 |
| 10 | How FET acts as voltage variable resistor | 1 | 4 | 1 |
| Part – B (Long Answer Questions) | | | | |
| 11 | a) With the help of a neat diagram explain the operation of an n-channel enhancement type MOSFET | 4 | 4 | 2 |
| | b) Detail the construction of an p-channel MOSFET of depletion type. Draw and explain its characteristics | 4 | 4 | 2 |
| 12 | a) Differentiate Enhancement MOSFET and Depletion MOSFET | 4 | 4 | 2 |
| | b) Explain drain and transfer characteristics of JFET | 3 | 4 | 3 |
| 13 | Why the input impedance in FET is very high in comparison with BJT? | 2 | 4 | 1 |
| 14 | a) Illustrate the working mechanism of JFET with necessary diagram | 4 | 4 | 3 |
| | b) What is the relation among FET parameters | 3 | 4 | 3 |

your roots to success...

UNIT-V

| S.No | Questions | BT | CO | PO | |
|--|---|---|----|----|---|
| Part – A (Short Answer Questions) | | | | | |
| 1 | Draw zener diode characteristics | 2 | 5 | 1 | |
| 2 | Write the applications of photo diode | 2 | 5 | 1 | |
| 3 | Write a short notes on varactor diode | 2 | 5 | 1 | |
| 4 | Explain voltage regulation using Zener diode | 2 | 5 | 1 | |
| 5 | What is regulation | 2 | 5 | 1 | |
| 6 | What are the applications of UJT | 2 | 5 | 2 | |
| 7 | Draw V-I characteristics of UJT and explain graph | 2 | 5 | 2 | |
| 8 | Write short notes on SCR | 2 | 5 | 2 | |
| 9 | Write short note on LED | 2 | 5 | 2 | |
| 10 | Write short notes on Schottky diode | 2 | 5 | 1 | |
| Part – B (Long Answer Questions) | | | | | |
| 11 | a) | Write short notes on varactor diode | 3 | 5 | 2 |
| | b) | Describe the construction and working of UJT with its equivalent circuit and V-I characteristics | 4 | 5 | 2 |
| 12 | a) | Distinguish between Avalanche and Zener breakdown | 2 | 5 | 2 |
| | b) | Explain about silicon-controlled rectifier | 3 | 5 | 2 |
| 13 | a) | With neat diagram explain the operation of zener diode and its forward and reverse characteristics | 3 | 5 | 1 |
| | b) | Mention some advantages and disadvantages of tunnel diode | 2 | 5 | 1 |
| 14 | a) | Explain the tunneling phenomenon in detail | 4 | 5 | 2 |
| | b) | Describe the principle of operation of tunnel diode | 4 | 5 | 2 |
| 15 | a) | Explain the working of semiconductor photo diode | 4 | 5 | 2 |
| | b) | Explain static characteristics of SCR | 4 | 5 | 2 |
| 16 | a) | Define varactor diode? Explain the operation of varactor diode with its equivalent circuit and mention its applications | 4 | 5 | 2 |
| | b) | With the help of V-I characteristics, explain SCR operation | 4 | 5 | 2 |

your roots to success...

R15

Code No: 123AU

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
B.Tech II Year I Semester Examinations, March - 2017**ELECTRONIC DEVICES AND CIRCUITS**
(Common to CSE, ECE, EEE, EIE, ETM, IT, MCT)**Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

- Part A is compulsory which carries 25 marks. Answer all questions in Part A.
Part B consists of 5 Units. Answer any one full question from each unit.
Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(25 Marks)**

- 1.a) Draw Zener Diode Characteristics. [2]
- b) Draw the Diode Equivalent Circuit. Mention the applications of PN-junction diode. [3]
- c) Explain how P-N junction diode acts as a Rectifier. [2]
- d) Explain the necessity of filter circuit after the rectifier circuit. [3]
- e) Explain how transistor work as an amplifier. [2]
- f) Compare CE,CC and CB configurations. [3]
- g) What is the need of biasing? [2]
- h) Explain Bias Compensation using Diodes. [3]
- i) Compare BJT and FET. [2]
- j) How FET acts as Voltage Variable Resistor? [3]

PART-B**(50 Marks)**

- 2.a) Explain the Avalanche and Zener Breakdowns in PN junction diode.
- b) What is tunneling phenomena? Explain the principle of operation of tunnel diode with its characteristics. [5+5]

OR

- 3.a) Derive the expression for transition capacitance of a diode.
 - b) Define varactor diode? Explain the operation of varactor diode with its equivalent circuit and mention its applications. [5+5]
4. A sinusoidal voltage whose $V_m=26V$ is applied to half-wave rectifier. The diode may be considered to be ideal and $R_L=1.2 K\Omega$ is connected as load. Find out peak value of current, RMS value of Current, DC value of current and Ripple factor. [10]

OR

- 5.a) Derive the expression for Ripple factor for Full Wave Rectifier with L-section filter.
- b) Compare FWR and Bridge rectifier. [5+5]

6. The reverse leakage current of the transistor when in CB configuration is $0.3\mu\text{A}$ while it is $16\mu\text{A}$ when the same transistor is connected in CE configuration. Determine α , β and γ . [10]

OR

- 7.a) Explain input and output characteristics of transistor in CB configuration with neat diagram.
b) Discuss the base width modulation. [5+5]
- 8.a) Derive the operating point using AC and DC load lines.
b) Draw the circuit diagram of a voltage divider bias and derive expression for Stability factor. [4+6]

OR

9. Draw the circuit diagram of CC amplifier using hybrid parameters and derive the expression for A_i , A_v , R_i and R_o . [10]
10. Explain the different biasing techniques of JFET. [10]

OR

11. Describe the construction and working principle of Enhancement mode and depletion mode MOSFET and draw its characteristics. [10]